 


CMSC 132 2nd Semester, 2014-2015

Exercise 3: Combinational Circuit Design in VHDL

1. Create **your own** logic circuit design for a **4:2 Priority Encoder**. Simplify your design by using Boolean Algebra or K-Map. **Write** your names, student numbers, lab section and solution on a sheet of yellow pad paper. Don't forget to include the truth table for the circuit as part of your solution.
2. Create VHDL program (Structural Design) and a test bench code for your solution. Then, simulate your work using GTKWave. Use `std_logic_vector` type for your input and encode output.
3. Create a VHDL program (Behavioral Design) and test bench for a 8:3 Priority Encoder. Simulate your work using GTKWave. Use `std_logic_vector` type for your input and encode output.



4. Don't forget to **document** (**comment**) your codes. Failure to do so will earn you some deductions.
5. This exercise is to be done in **pairs**. If you have any questions or clarifications, feel free to e-mail or consult your lab instructor.
6. Submission details:
 - Deadline for the submission of your written solution will be five **(5)** days after this exercise was given to your lab section.
 - Store your **VHDL codes** inside a ZIP file. Name your ZIP file as "surname1_surname2_labsection_exer3.zip". Example: *bautista_surname2_t-4l_e3.zip*Create separate folders for the 8:3 and 4:2 Priority Encoders.
- Submit your .zip file via schoolology.com. Note: All members must submit a copy of the exercise on their respective Schoolology accounts.
- You are required to present your VHDL codes.