


CMSC 130 – Logic Design and Digital Computer Circuits

Handout # 5: DESIGN OF COMBINATIONAL CIRCUITS


Fundamental Components of Digital Systems

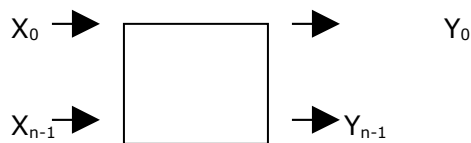- 1.) Combinatorial Logic Blocks (Functions)
- 2.) State Elements (Memory)
- 3.) Interconnect (wires)

Combinatorial Circuit – consists of logic gates whose outputs at a time are determined from the present combination of inputs without regards to the previous inputs.




each input/output is a single bit.

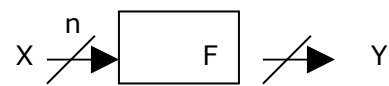

$Y = F(X_1, X_2, \dots, X_{n-1})$ where x, y are $\{0,1\}$

ex. 4-bit adder

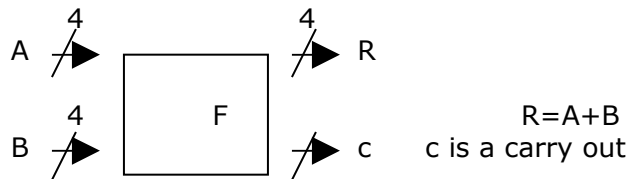

Truth Table Representation :

a3	a2	a1	a0	b3	b2	b1	b0	r3	r2	r1	r0	c
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1	0	0	1	0	0
0	0	1	0	0	0	1	0	0	1	0	0	0
0	0	1	1	0	0	1	1	0	1	1	0	0
...												
0	0	1	0	0	0	1	0	0	1	0	0	0
0	0	1	0	0	0	1	1	0	1	0	1	0
...												
0	0	0	0	1	1	1	1	1	1	1	1	0
0	0	0	1	1	1	1	1	0	0	0	0	1

-> 256 rows! In general, 2^n rows for n inputs.

	a3	a2	a1	a0
+	b3	b2	b1	b0
<hr/>				
c	r3	r2	r1	r0

Add a_0 and b_0 as follows:

a	b	sum	C _{out}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


sum = a XOR b
C_{out} = a AND b
= ab

Add a_0 and b_0 as follows: carry to next column


C _{in}	a _i	b _i	sum _i	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

sum_i = a_i XOR b_i XOR C_{in}
C_{out} = a_ib_i + a_iC_{in} + b_iC_{in}

Full Adder Cell

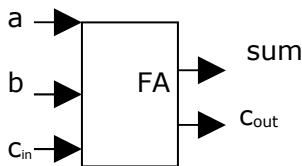

The 4-bit adder :

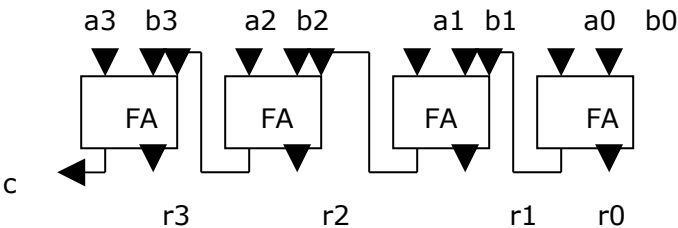

Example: BCD-to-Excess3 code converter

Truth Table

BCD				XS-3			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
...							
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
...							
1	1	1	1	X	X	X	X

AB\CD	00	01	11	10
D				
00	1			1
01	1			1
11	X	X	X	X
10	1		X	X

$z = d'$

AB\CD	00	01	11	10
00	1		1	
01	1		1	
11	X	X	X	X
10	1		X	X

$y = cd + c'd'$

AB\CD	00	01	11	10
00		1	1	1
01	1			
11	X	X	X	X
10		1	X	X

$x = b'c + b'd + bc'd'$

AB\CD	00	01	11	10
00				
01		1	1	1
11	X	X	X	X
10	1	1	X	X

$w = a + bc + bd$

Functions for the BCD-to-XS3 Converter:

$$\begin{aligned} z &= d' & y &= cd + c'd' \\ x &= b'c + b'd + bc'd' & w &= a + bc + bd \end{aligned}$$

Note: The functions are algebraically manipulated for the purpose of using common gates for two or more outputs.

Logic Diagram of the BCD-to-XS3 Converter:

