 


## CMSC 130 – Logic Design and Digital Computer Circuits

### Handout # 8: SYNCHRONOUS SEQUENTIAL LOGIC – FLIP-FLOPS



**Block Diagram of a Sequential Circuit**

#### Sequential circuit

- consists of a combinational circuit to which memory elements are connected to form a feedback path
- memory elements – store binary info which defines the *state* of the sequential circuit
- output – is determined by the external inputs and the present state
- next state of the memory elements – is a function of external inputs and the present state
- hence, a sequential circuit is a time sequence of inputs, outputs, and internal states
- *synchronous* – a system whose behavior can be defined from the knowledge of its signals at discrete instants of time
- *asynchronous* – depends upon the order in which its input signals change and can be affected at any instant of time

#### Synchronous Sequential Logic Systems

- *master-clock generator* – timing device used for synchronization; generates a periodic train of *clock pulses*
- memory elements are affected only upon the arrival of the synchronization pulse
- *clocked sequential circuits* – synchronous sequential circuits that use clock pulses in the inputs of memory elements

#### Flip-Flops

- memory elements used in clocked sequential circuits

- binary cells capable of storing one bit of info
- flip-flop circuits have two inputs, normal and complemented
- A flip-flop circuit can maintain a binary state indefinitely (as long as power is delivered to the circuit) until directed by an input signal to switch states.

#### Flip-Flop Characteristic Tables

| JK Flip-Flop |   |        |            |
|--------------|---|--------|------------|
| J            | K | Q(t+1) | Operation  |
| 0            | 0 | Q(t)   | no change  |
| 0            | 1 | 0      | reset      |
| 1            | 0 | 1      | set        |
| 1            | 1 | Q'(t)  | complement |


| SR Flip-Flop |   |        |               |
|--------------|---|--------|---------------|
| S            | R | Q(t+1) | Operation     |
| 0            | 0 | Q(t)   | no change     |
| 0            | 1 | 0      | reset         |
| 1            | 0 | 1      | set           |
| 1            | 1 | ?      | indeterminate |

| D Flip-Flop (Data) |        |           |
|--------------------|--------|-----------|
| D                  | Q(t+1) | Operation |
| 0                  | 0      | reset     |
| 1                  | 1      | set       |


| T Flip-Flop (Toggle) |        |            |
|----------------------|--------|------------|
| T                    | Q(t+1) | Operation  |
| 0                    | Q(t)   | no change  |
| 1                    | Q'(t)  | complement |
 
## Triggering of Flip-Flops

- *trigger* - a momentary change in the input signal which switches the state of a flip-flop
- *clock pulse* - triggers clocked flip-flops; starts from an initial value of 0, goes momentarily to 1, and after a short time, returns to its initial 0 value; may be positive or negative
- *positive clock pulse* - remains at 0 during the interval between pulses and goes to 1 during the occurrence of a pulse
- the clock pulse goes through two signal transitions: from 0 to 1 and the return from 1 to 0
- positive transition is defined as the *positive edge*, negative transition as the *negative edge*




Definition of clock-pulse transition

 

Timing Diagram of a JK Flip-Flop

 
## Master-Slave Flip-Flop

- consists of two latches (master and slave) and an inverter



Master-Slave D Flip-Flop

- when the clock pulse input C is 0, the output of the slave latch is enabled and its output Q is equal to the master output Y, master latch is disabled (its C input = 0)
- when the input pulse changes to the logic-1 level, the data in the external D input is transferred to the master
- the slave is disabled as long as the pulse remains in the 1 level (its C input = 1)
- any changes in the external D input changes the master output Y but cannot affect the slave output Q
- when the pulse returns to 0, the master is disabled and is isolated from the D input
- at the same time, the slave is enabled and the value of Y is transferred to the output of the flip-flop at Q

 

Timing Relationship with a Master-Slave Flip-Flop