

Chapter 3

Boolean Algebra, Logic Functions, and Logic Gates (Part 2)

Binary Variables

- Forms of variables
 - normal (x)
 - complement (x')
- Forms of terms (variables x and y)
 - Minterms m_i (or standard product)
$$x'y', x'y, xy', xy$$
 - Maxterms M_i (or standard sum)
$$x+y, x+y', x'+y, x'+y'$$

Minterms and Maxterms for 3 variables

			MINTERM		MAXTERM	
x	y	z	Term	Designation	Term	Designation
0	0	0		m0		M0
0	0	1		m1		M1
0	1	0		m2		M2
0	1	1		m3		M3
1	0	0		m4		M4
1	0	1		m5		M5
1	1	0		m6		M6
1	1	1		m7		M7

Minterms and Maxterms for 3 variables

			MINTERM		MAXTERM	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m0		M0
0	0	1	$x'y'z$	m1		M1
0	1	0	$x'yz'$	m2		M2
0	1	1	$x'yz$	m3		M3
1	0	0	$xy'z'$	m4		M4
1	0	1	$xy'z$	m5		M5
1	1	0	xyz'	m6		M6
1	1	1	xyz	m7		M7

Minterms and Maxterms for 3 variables

			MINTERM		MAXTERM	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m0	$x+y+z$	M0
0	0	1	$x'y'z$	m1	$x+y+z'$	M1
0	1	0	$x'yz'$	m2	$x+y'+z$	M2
0	1	1	$x'yz$	m3	$x+y'+z'$	M3
1	0	0	$xy'z'$	m4	$x'+y+z$	M4
1	0	1	$xy'z$	m5	$x'+y+z'$	M5
1	1	0	xyz'	m6	$x'+y'+z$	M6
1	1	1	xyz	m7	$x'+y'+z'$	M7

Forms of Boolean Functions

- Canonical Form
 - Sum of minterms
 - Product of maxterms
- Standard Form
 - Sum of products
 - Product of sums

Forms of Boolean Functions

Examples

- $F(a,b,c) = abc' + a'bc$
- $F(w,x,y,z) = (w+x'+y'+z)(x+y+z')$
- $F(x,y,z) = xz' + y$
- $F(a,b,c,d) = (a+b'+c+d)(a+b+c'+d')$

Sum of Minterms

- Any Boolean function can be expressed as a sum of minterms
- “sum” means Oring the minterms that produces a 1 in the function
- Each minterm is obtained from an AND term of the n variables, with each variable being primed if the corresponding bit of the binary number is a 0 and unprimed if a 1.

Example – Truth Table

Express $F(A,B,C) = A + B'C$ in sum of minterms

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Example – Truth Table

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$\begin{aligned} &= A'B'C + AB'C' + AB'C + \\ &\quad ABC' + ABC \\ &= \Sigma (1, 4, 5, 6, 7) \end{aligned}$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$F = A(B+B') + B'C$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$\begin{aligned} F &= A(B+B') + B'C \\ &= AB + AB' + B'C \end{aligned}$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$\begin{aligned} F &= A(B+B') + B'C \\ &= AB + AB' + B'C \\ &= AB(C+C') + AB'(C+C') + B'C(A+A') \end{aligned}$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$F = A(B+B') + B'C$$

$$= AB + AB' + B'C$$

$$= AB(C+C') + AB'(C+C') + B'C(A+A')$$

$$= ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$\begin{aligned} F &= A(B+B') + B'C \\ &= AB + AB' + B'C \\ &= AB(C+C') + AB'(C+C') + B'C(A+A') \\ &= ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C \\ &= A'B'C + AB'C' + AB'C + ABC' + ABC \end{aligned}$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$\begin{aligned} F &= A(B+B') + B'C \\ &= AB + AB' + B'C \\ &= AB(C+C') + AB'(C+C') + B'C(A+A') \\ &= ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C \\ &= A'B'C + AB'C' + AB'C + ABC' + ABC \\ &= m_1 + m_4 + m_5 + m_6 + m_7 \\ &= \Sigma (1, 4, 5, 6, 7) \end{aligned}$$

Product of Maxterms

- Any Boolean function can be expressed as a product of maxterms
- “product” means ANDing the maxterms that produces a 0 in the function
- Each maxterm is obtained from OR term of the n variables, with each variable being primed if the corresponding bit of the binary number is a 1 and unprimed if a 0.

Example – Truth Table

Express $F(A,B,C) = A + B'C$ in product of maxterms

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Example – Truth Table

Express $F(A,B,C) = A + B'C$ in product of maxterms

$$= (A+B+C)(A+B'+C)(A+B'+C')$$

$$= \Pi(0, 2, 3)$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in product of maxterms

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in product of maxterms

$$F = (A+B')(A+C)$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in product of maxterms

$$\begin{aligned} F &= (A+B')(A+C) \\ &= (A+B'+CC')(A+C) \end{aligned}$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in product of maxterms

$$\begin{aligned} F &= (A+B')(A+C) \\ &= (A+B'+CC')(A+C) \\ &= (A+B'+C)(A+B'+C')(A+C+BB') \end{aligned}$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in product of maxterms

$$\begin{aligned} F &= (A+B')(A+C) \\ &= (A+B'+CC')(A+C) \\ &= (A+B'+C)(A+B'+C')(A+C+BB') \\ &= (A+B'+C)(A+B'+C')(A+B+C)(A+B'+C) \end{aligned}$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in product of maxterms

$$\begin{aligned} F &= (A+B')(A+C) \\ &= (A+B'+CC')(A+C) \\ &= (A+B'+C)(A+B'+C')(A+C+BB') \\ &= (A+B'+C)(A+B'+C')(A+B+C)(A+B'+C) \\ &= (A+B+C)(A+B'+C)(A+B'+C') \end{aligned}$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in product of maxterms

$$\begin{aligned} F &= (A+B')(A+C) \\ &= (A+B'+CC')(A+C) \\ &= (A+B'+C)(A+B'+C')(A+C+BB') \\ &= (A+B'+C)(A+B'+C')(A+B+C)(A+B'+C) \\ &= (A+B+C)(A+B'+C)(A+B'+C') \\ &= M_0 M_2 M_3 \\ &= \Pi(0, 2, 3) \end{aligned}$$

Conversion between Canonical forms

- Consider the previous example: $F = A + B'C$

$$F(A,B,C) = \Sigma(1, 4, 5, 6, 7)$$


This has a complement that can be expressed as:

$$F'(A,B,C) = \Sigma(0, 2, 3) = m_0 + m_2 + m_3$$


Now, take the complement of F' , we will obtain

$$\begin{aligned} F &= (m_0 + m_2 + m_3)' = m_0' m_2' m_3' = M_0 M_2 M_3 \\ &= \Pi(0, 2, 3) \end{aligned}$$


Digital Logic Gates

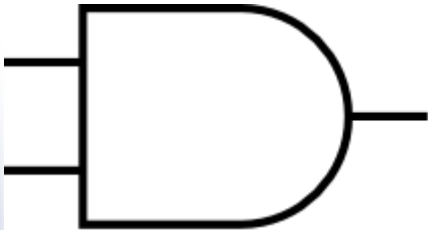


AND Gate

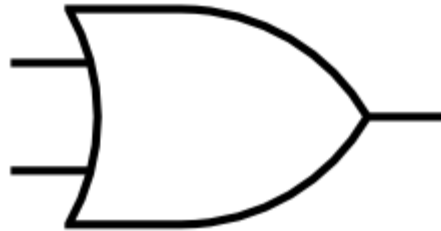


OR Gate

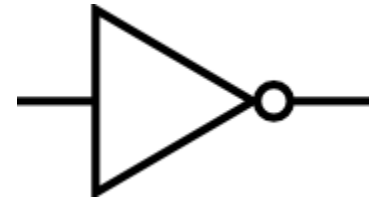


NOT Gate

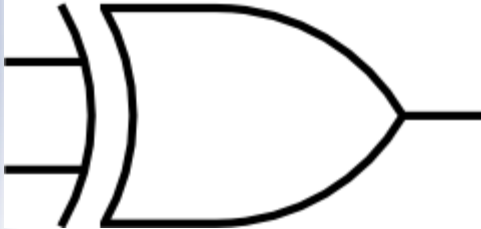

XOR Gate

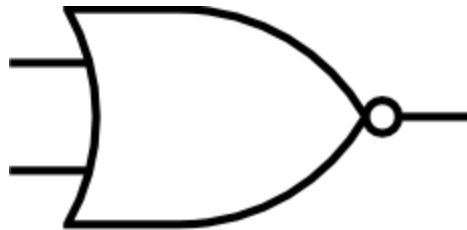

NOR Gate

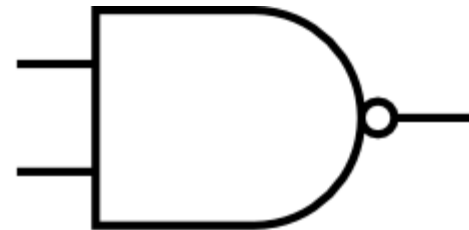


NAND Gate



XNOR Gate


AND Gate

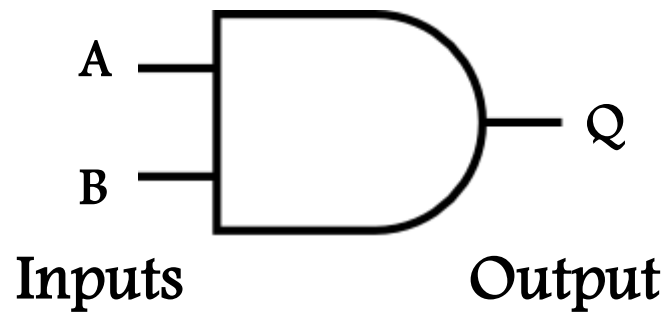

Truth Table

Inputs		Output
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate

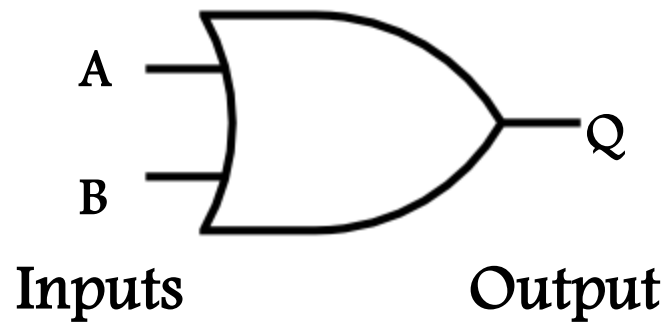


Truth Table

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

NOT Gate

Truth Table

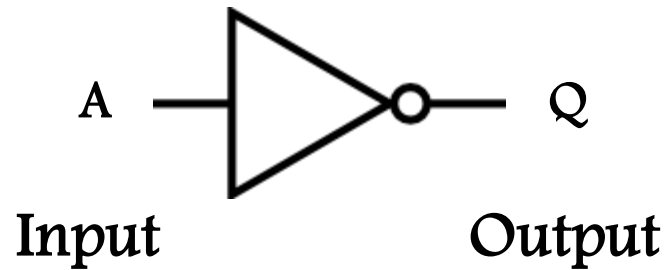

Input	Output
A	Q
0	1
1	0

Other Gates


- Why use?
 - Saves cost
 - Saves space
 - Saves time

Other Gates

- Why use?
 - Saves cost
 - Saves space
 - Saves time
- Types
 - NAND gate
 - NOR gate
 - XOR gate
 - XNOR gate

NAND Gate


Truth Table

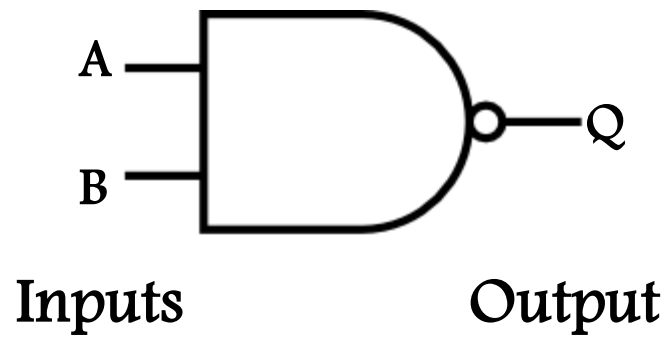

Inputs		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

NOR Gate


Truth Table

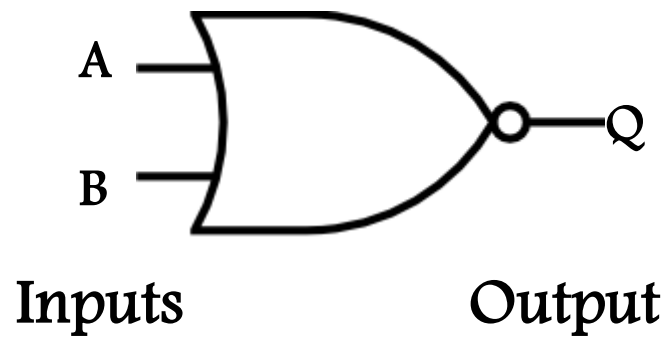

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0

Exclusive-OR Gate


Truth Table

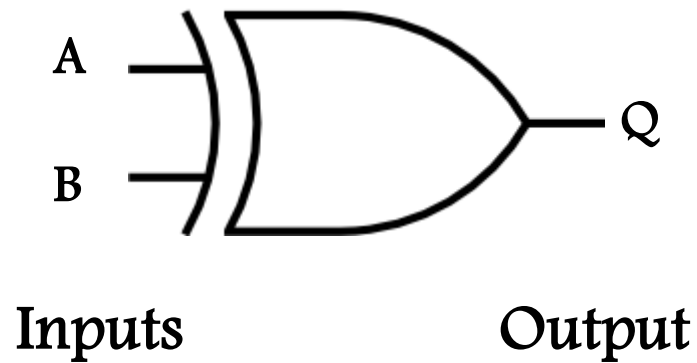

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

XNOR Gate

Truth Table

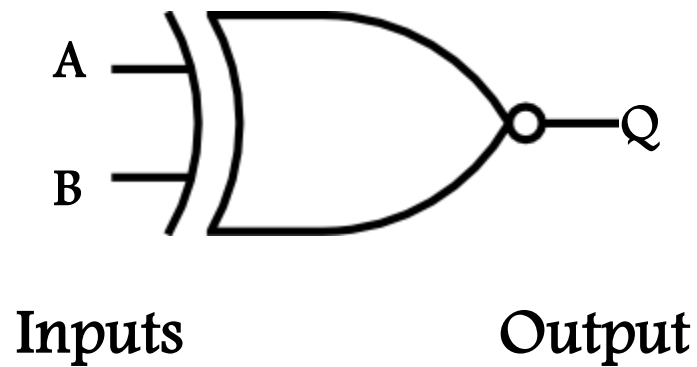

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

Digital Logic gates

- Draw the logic diagram of the function
 $F = A + B'C$


A

B

C


Digital Logic gates

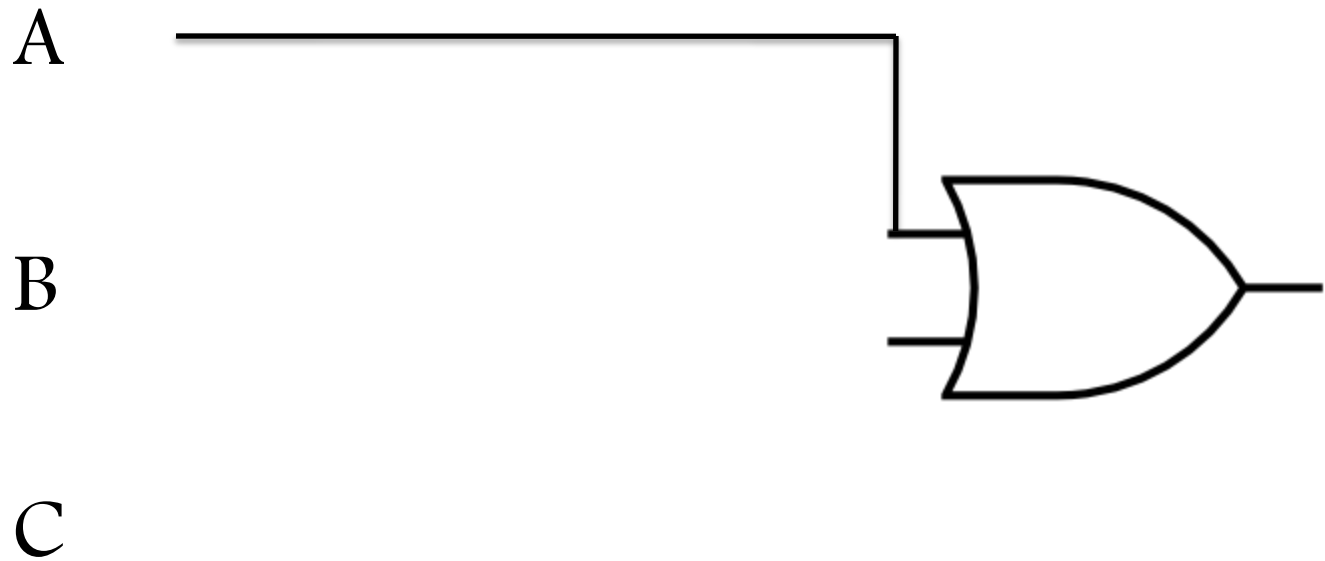- Draw the logic diagram of the function
 $F = A + B'C$




Digital Logic gates

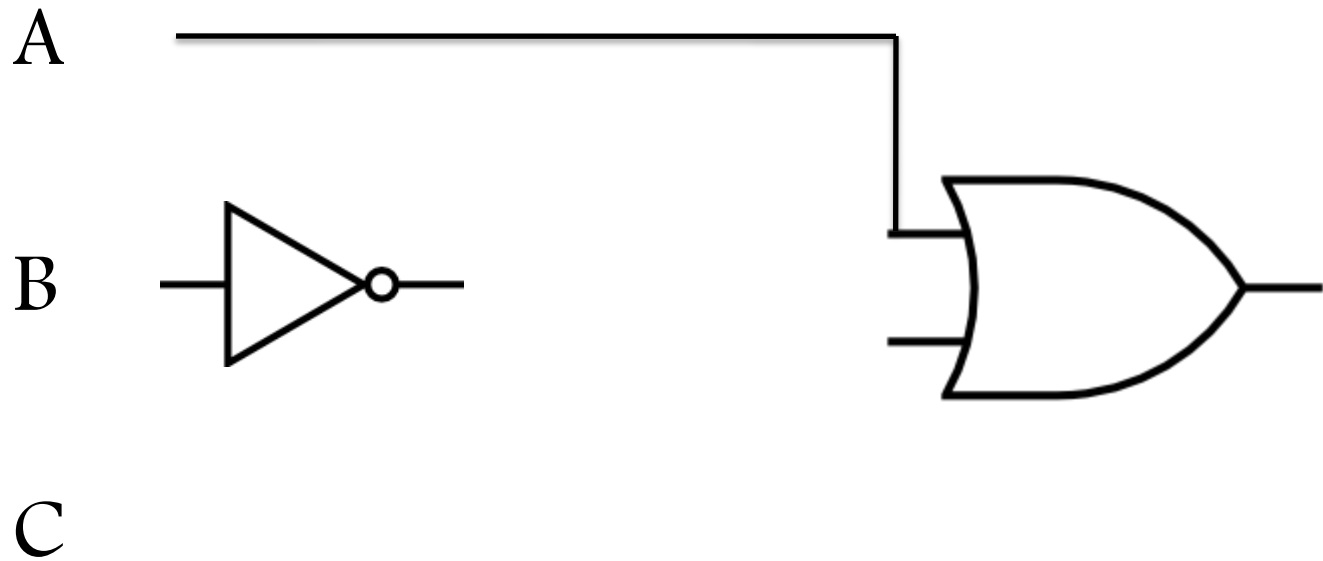- Draw the logic diagram of the function $F = A + B'C$




Digital Logic gates

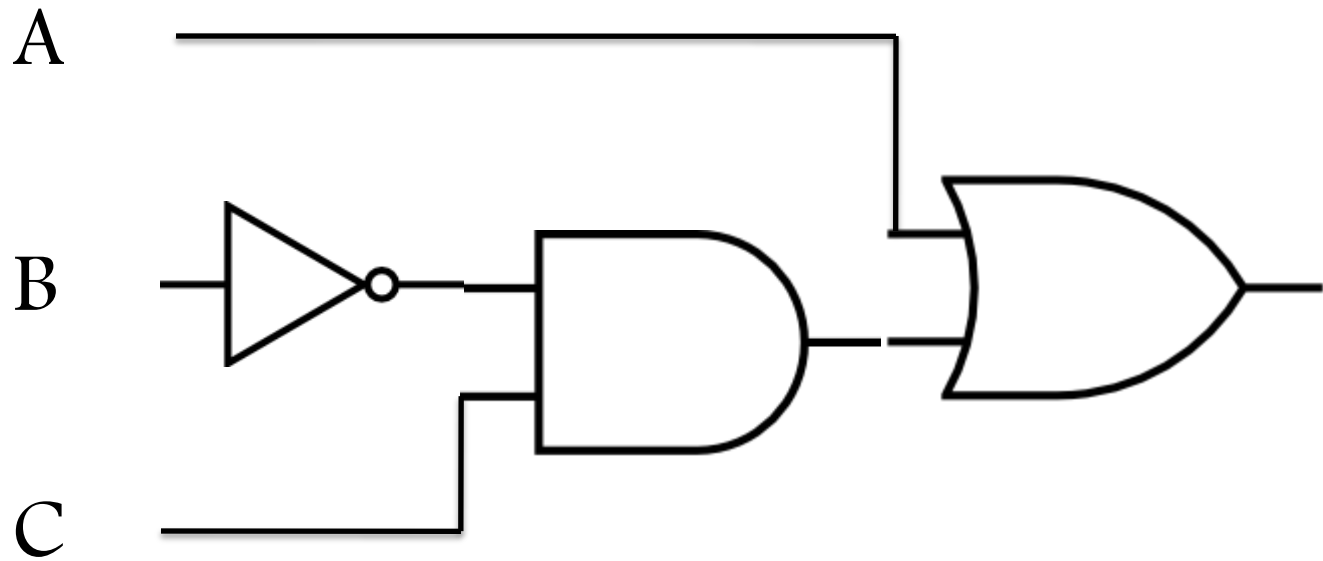- Draw the logic diagram of the function $F = A + B'C$




Digital Logic gates

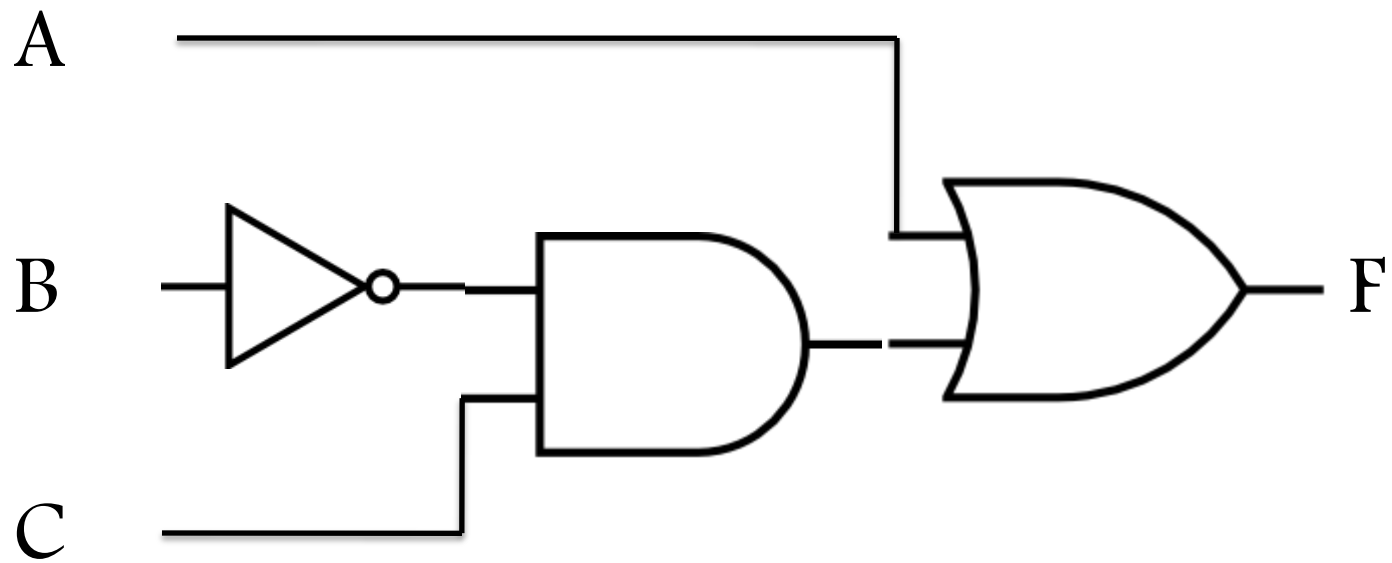
- Draw the logic diagram of the function $F = A + B'C$





Universality of a NAND gate

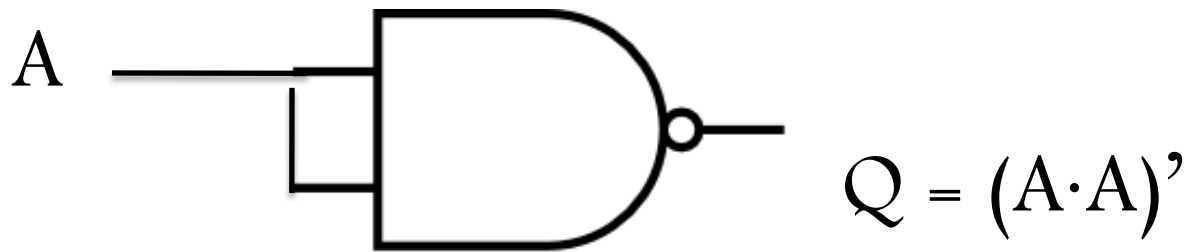

Universality of a NAND gate

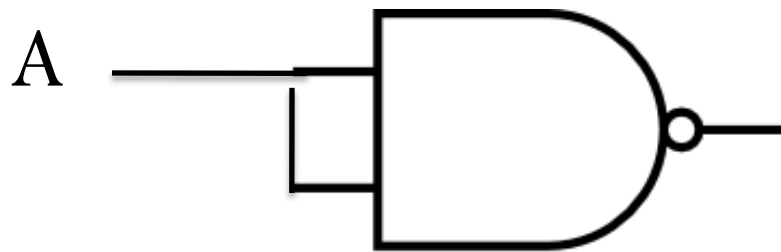


$$Q = (A \cdot A)'$$

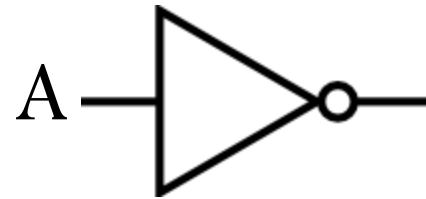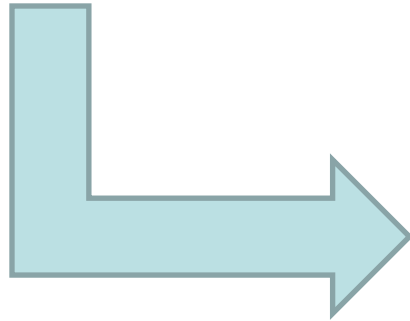


$$Q = A'$$

Universality of a NAND gate

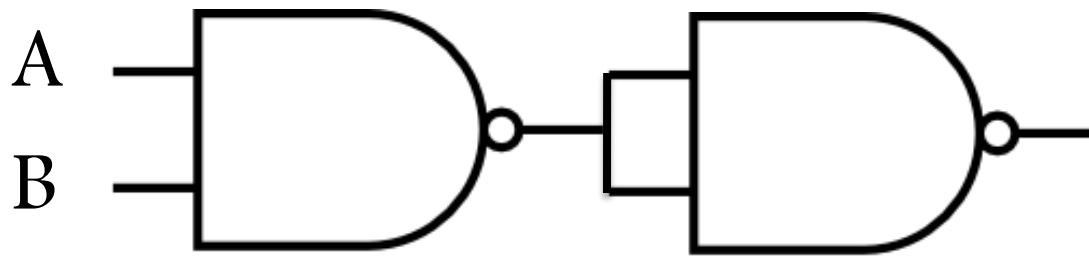


Universality of a NAND gate

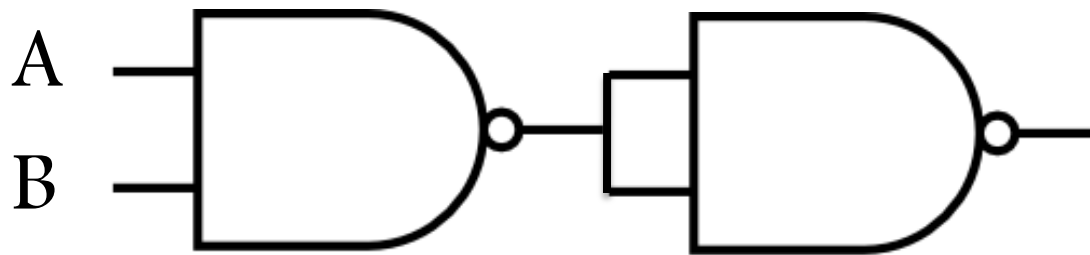


$$Q = ((AB)'(AB)')'$$


Universality of a NAND gate

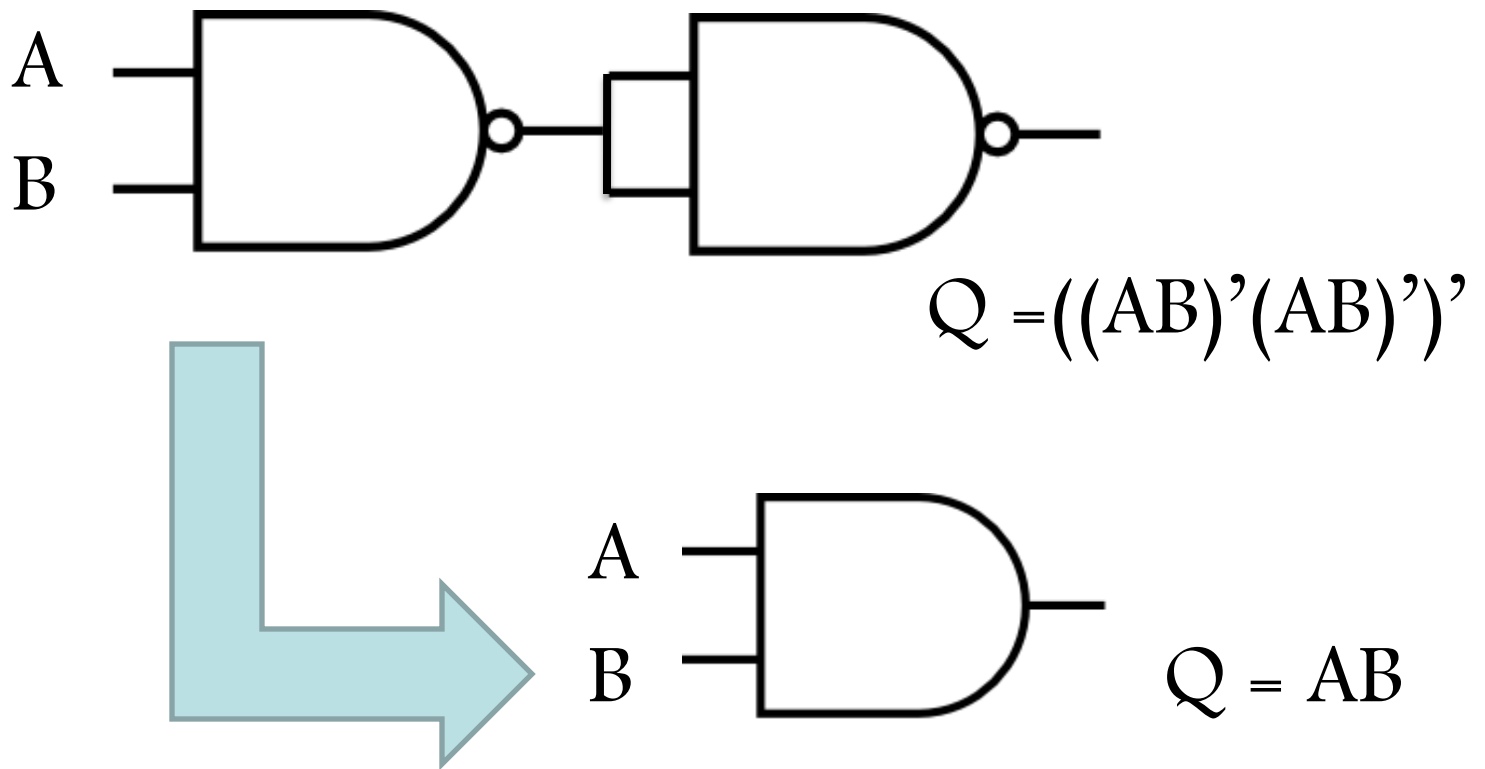




Universality of a NAND gate

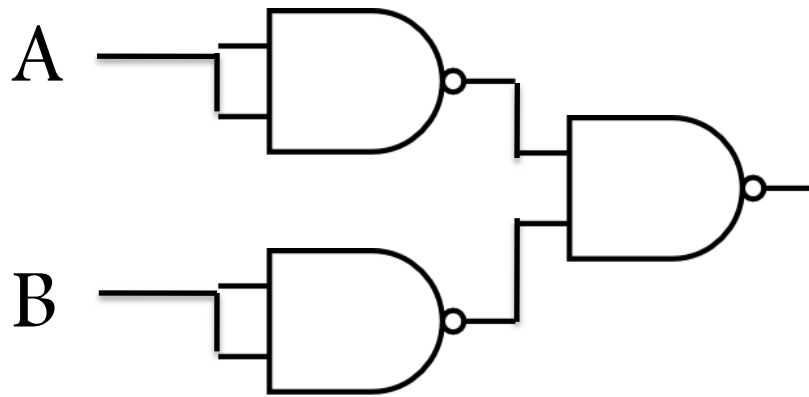


Universality of a NAND gate

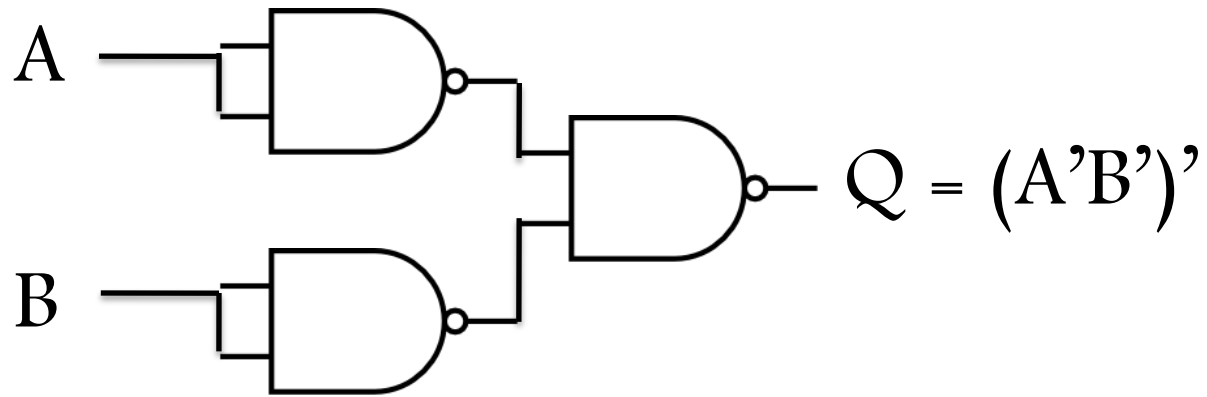

Universality of a NAND gate

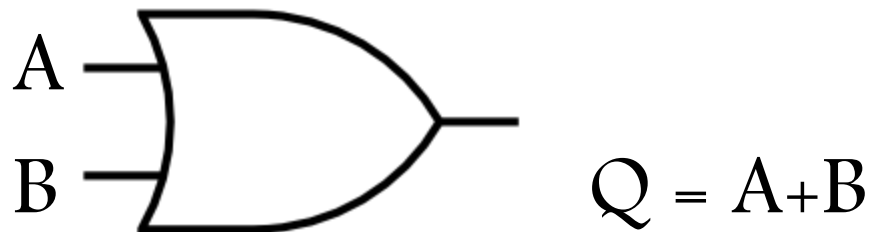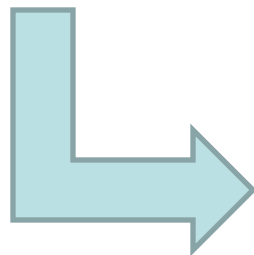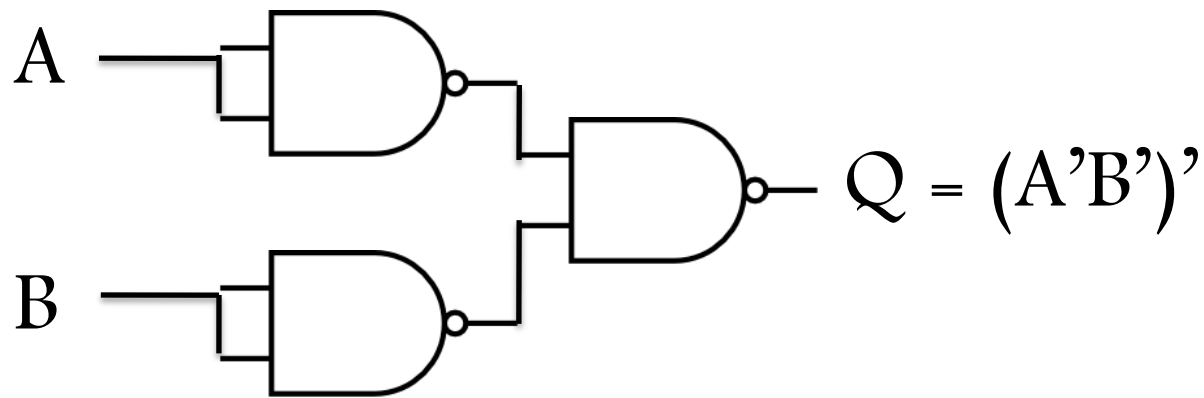


Universality of a NOR gate


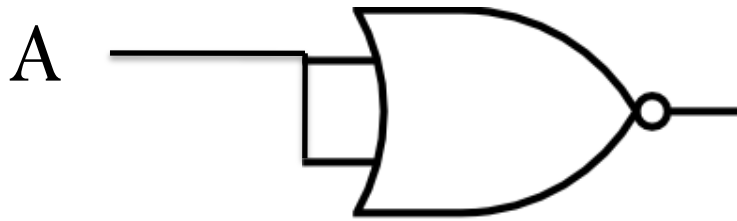


$$Q = (A+A)'$$

Universality of a NOR gate

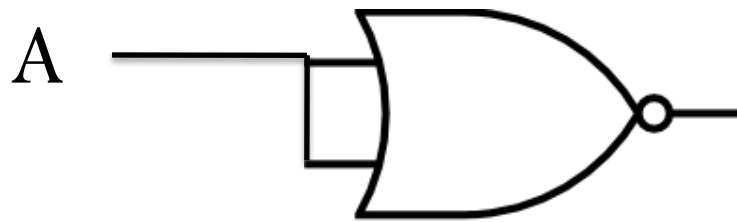


$$Q = (A + A)'$$

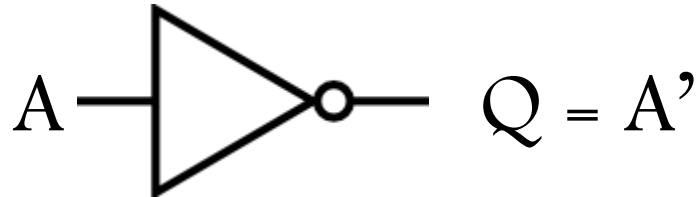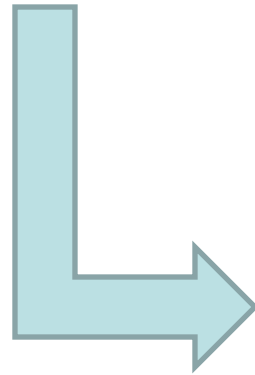


$$Q = A'$$

Universality of a NOR gate

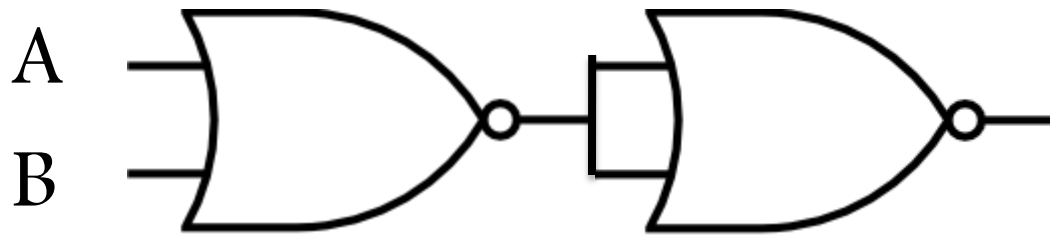


Universality of a NOR gate

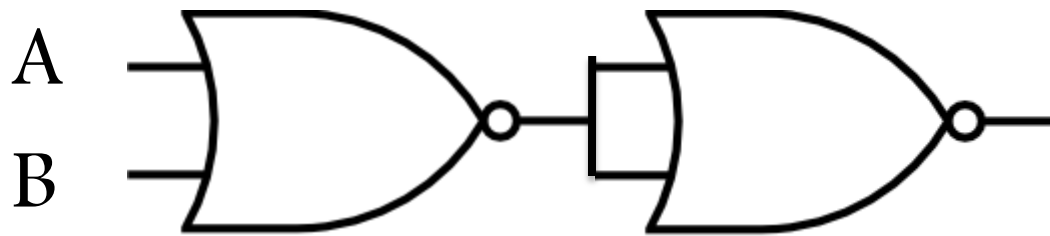


$$Q = ((A+B)' + (A+B)')'$$


Universality of a NOR gate

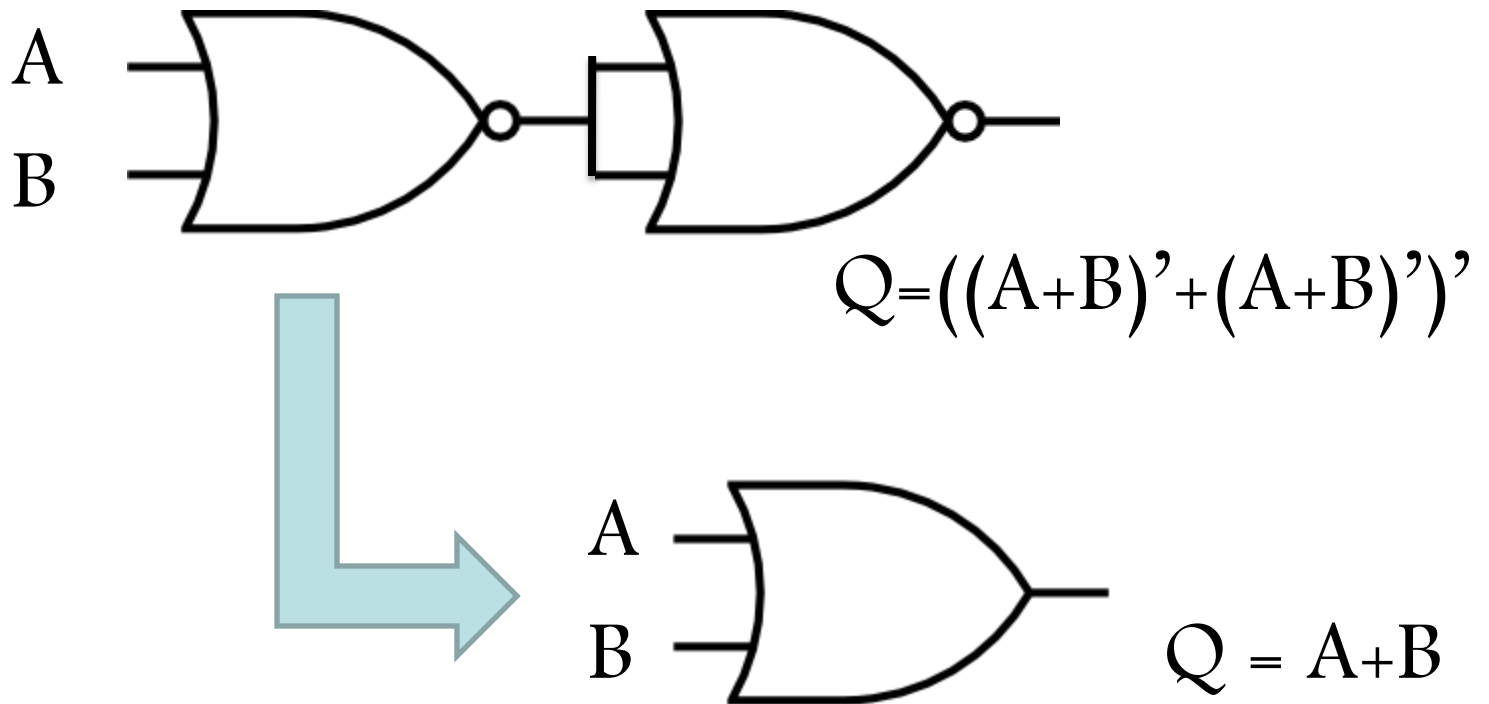


Universality of a NOR gate

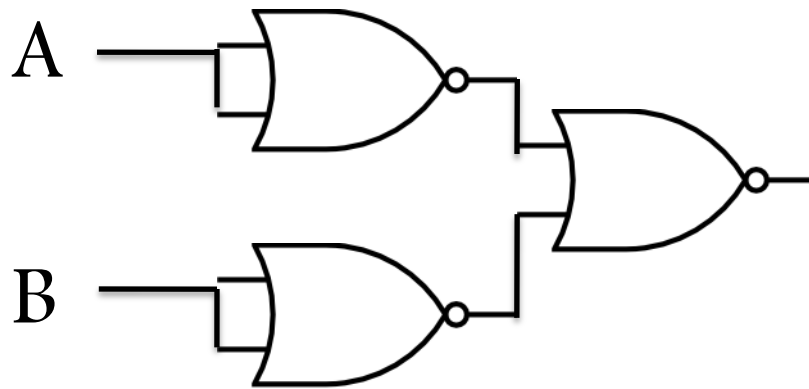

Universality of a NOR gate

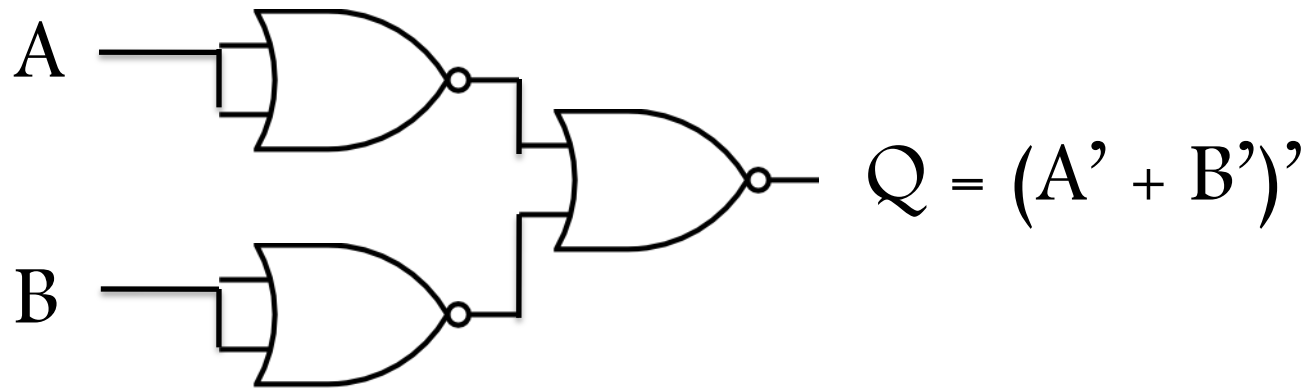


Universality of a NOR gate

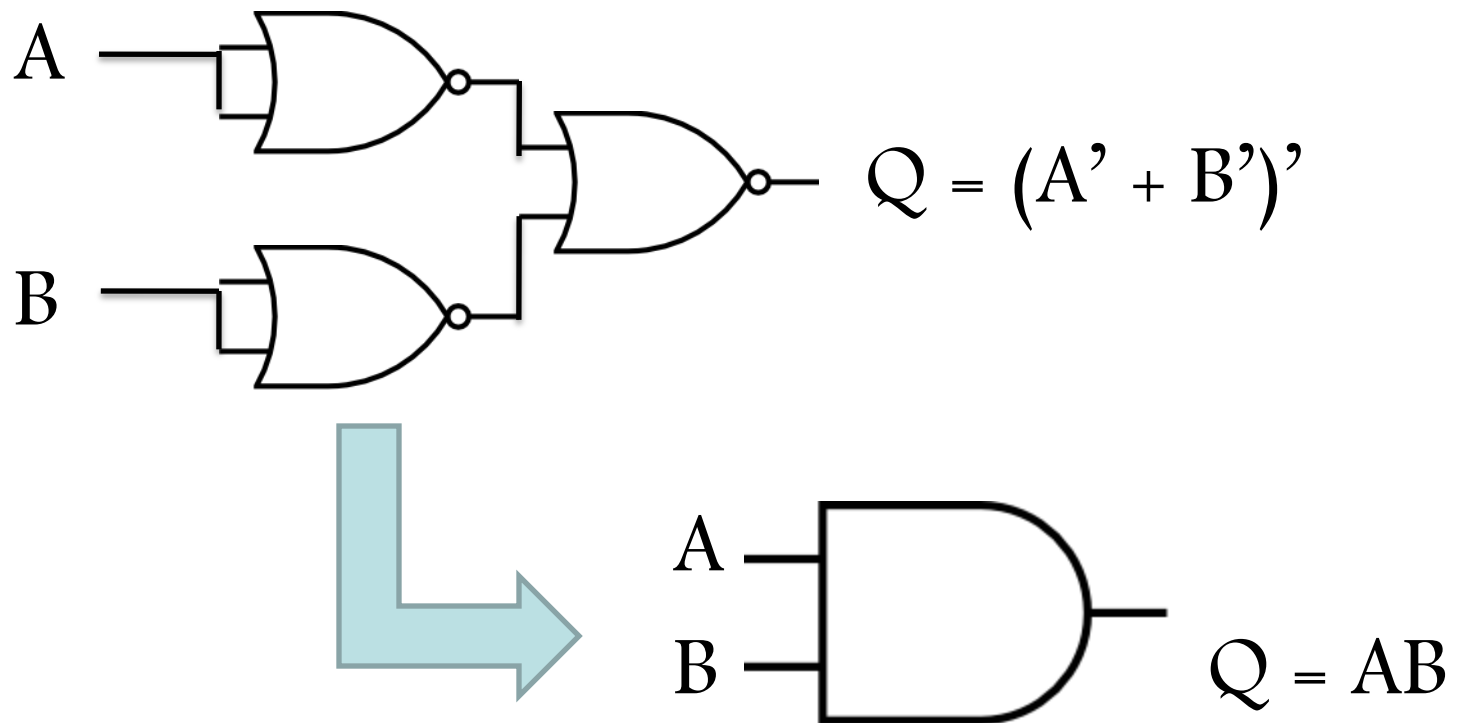

Real Gates

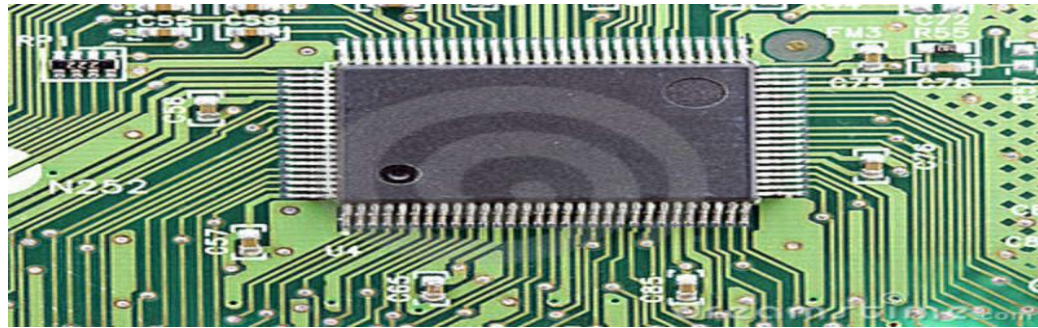- Logic gates are integrated form
 - Built within a solid piece of silicon called IC (Integrated Circuit)



- Several gates are included in a single plastic moulding

IC Families

- Transistor–Transistor Logic (TTL)
- Emitter Coupled Logic (ECL)
- Complementary Metal–Oxide–Semiconductor (CMOS)

Levels of IC

- Small-scale Integration
 - ICs with 1 to 10 gates
- Medium-scale Integration
 - ICs with 10 to 100 gates
- Large-scale Integration
 - ICs with 100 to 1000s of gates
- Very large-scale Integration
 - ICs with 1000s to millions of gates