



Chapter 3

BOOLEAN ALGEBRA, LOGIC FUNCTIONS and LOGIC GATES

Binary Variables

- Forms of variables
 - normal (x)
 - complement (x')
- Forms of terms (variables x and y)
 - Minterms m_i (or standard product)
$$x'y', x'y, xy', xy$$
 - Maxterms M_i (or standard sum)
$$x+y, x+y', x'+y, x'+y'$$

Minterms and Maxterms for 3 variables

			MINTERM		MAXTERM	
x	y	z	Term	Designation	Term	Designation
0	0	0		m0		M0
0	0	1		m1		M1
0	1	0		m2		M2
0	1	1		m3		M3
1	0	0		m4		M4
1	0	1		m5		M5
1	1	0		m6		M6
1	1	1		m7		M7

Minterms and Maxterms for 3 variables

			MINTERM		MAXTERM	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m0		M0
0	0	1	$x'y'z$	m1		M1
0	1	0	$x'yz'$	m2		M2
0	1	1	$x'yz$	m3		M3
1	0	0	$xy'z'$	m4		M4
1	0	1	$xy'z$	m5		M5
1	1	0	xyz'	m6		M6
1	1	1	xyz	m7		M7

Minterms and Maxterms for 3 variables

			MINTERM		MAXTERM	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m0	$x+y+z$	M0
0	0	1	$x'y'z$	m1	$x+y+z'$	M1
0	1	0	$x'yz'$	m2	$x+y'+z$	M2
0	1	1	$x'yz$	m3	$x+y'+z'$	M3
1	0	0	$xy'z'$	m4	$x'+y+z$	M4
1	0	1	$xy'z$	m5	$x'+y+z'$	M5
1	1	0	xyz'	m6	$x'+y'+z$	M6
1	1	1	xyz	m7	$x'+y'+z'$	M7



Forms of Boolean Functions

- Canonical Form

- Sum of minterms
- Product of maxterms

- Standard Form

- Sum of products
- Product of sums

Forms of Boolean Functions

Examples

- $F(a,b,c) = abc' + a'bc$
- $F(w,x,y,z) = (w+x'+y'+z)(x+y+z')$
- $F(x,y,z) = xz' + y$
- $F(a,b,c,d) = (a+b'+c+d)(a+b+c'+d')$



Sum of Minterms

- Any Boolean function can be expressed as a sum of minterms
- “sum” means ORing the minterms that produces a 1 in the function
- Each minterm is obtained from an AND term of the n variables, with each variable being primed if the corresponding bit of the binary number is a 0 and unprimed if a 1.

Example – Truth Table

Express $F(A,B,C) = A + B'C$ in sum of minterms

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Example – Truth Table

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$\begin{aligned} &= A'B'C + AB'C' + AB'C + ABC' \\ &\quad + ABC \\ &= \Sigma (1, 4, 5, 6, 7) \end{aligned}$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1



Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms



Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$F = A(B+B') + B'C$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$F = A(B+B') + B'C$$

$$= AB + AB' + B'C$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$F = A(B+B') + B'C$$

$$= AB + AB' + B'C$$

$$= AB(C+C') + AB'(C+C') + B'C(A+A')$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$F = A(B+B') + B'C$$

$$= AB + AB' + B'C$$

$$= AB(C+C') + AB'(C+C') + B'C(A+A')$$

$$= ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$F = A(B+B') + B'C$$

$$= AB + AB' + B'C$$

$$= AB(C+C') + AB'(C+C') + B'C(A+A')$$

$$= ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C$$

$$= A'B'C + AB'C' + AB'C + ABC' + ABC$$

Example – Algebraic Manipulation

Express $F(A,B,C) = A + B'C$ in sum of minterms

$$F = A(B+B') + B'C$$

$$= AB + AB' + B'C$$

$$= AB(C+C') + AB'(C+C') + B'C(A+A')$$

$$= ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C$$

$$= A'B'C + AB'C' + AB'C + ABC' + ABC$$

$$= m_1 + m_4 + m_5 + m_6 + m_7$$

$$= \Sigma(1, 4, 5, 6, 7)$$



Product of Maxterms

- Any Boolean function can be expressed as a product of maxterms
- “product” means ANDing the maxterms that produces a 0 in the function
- Each maxterm is obtained from an OR term of the n variables, with each variable being primed if the corresponding bit of the binary number is a 1 and unprimed if a 0.

Example – Truth Table

Express $F(A,B,C) = A + B'C$ in product of maxterms

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Example – Truth Table

Express $F(A,B,C) = A + B'C$ in product of maxterms

$$= (A+B+C)(A+B'+C)(A+B'+C')$$

$$= \Pi(0,2,3)$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1



Example – Algebraic Manipulation

Express $F = A + B'C$ in product of maxterms



Example – Algebraic Manipulation

Express $F = A + B'C$ in product of maxterms

$$F = (A+B')(A+C)$$



Example – Algebraic Manipulation

Express $F = A + B'C$ in product of maxterms

$$F = (A+B')(A+C)$$

$$= (A+B'+CC')(A+C)$$

Example – Algebraic Manipulation

Express $F = A + B'C$ in product of maxterms

$$F = (A+B')(A+C)$$

$$= (A+B'+CC')(A+C)$$

$$= (A+B'+C)(A+B'+C')(A+C+BB')$$

Example – Algebraic Manipulation

Express $F = A + B'C$ in product of maxterms

$$F = (A+B')(A+C)$$

$$= (A+B'+CC')(A+C)$$

$$= (A+B'+C)(A+B'+C')(A+C+BB')$$

$$= (A+B'+C)(A+B'+C')(A+B+C)(A+B'+C)$$

Example – Algebraic Manipulation

Express $F = A + B'C$ in product of maxterms

$$F = (A+B')(A+C)$$

$$= (A+B'+CC')(A+C)$$

$$= (A+B'+C)(A+B'+C')(A+C+BB')$$

$$= (A+B'+C)(A+B'+C')(A+B+C)(A+B'+C)$$

$$= (A+B+C)(A+B'+C)(A+B'+C')$$

Example – Algebraic Manipulation

Express $F = A + B'C$ in product of maxterms

$$F = (A+B')(A+C)$$

$$= (A+B'+CC')(A+C)$$

$$= (A+B'+C)(A+B'+C')(A+C+BB')$$

$$= (A+B'+C)(A+B'+C')(A+B+C)(A+B'+C)$$

$$= (A+B+C)(A+B'+C)(A+B'+C')$$

$$= M_0 M_2 M_3$$

$$= \Pi(0,2,3)$$

Conversion between Canonical forms

- Consider the previous example: $F = A + B'C$

$$F(A,B,C) = \Sigma(1,4,5,6,7)$$

This has a complement that can be expressed as:

$$F'(A,B,C) = \Sigma(0,2,3) = m_0 + m_2 + m_3$$

Now, take the complement of F' , we will obtain

$$\begin{aligned} F &= (m_0 + m_2 + m_3)' = m_0' m_2' m_3' = M_0 M_2 M_3 \\ &= \Pi(0,2,3) \end{aligned}$$


Digital Logic Gates



AND gate



OR gate

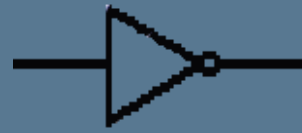

NOT gate



XOR gate



NOR gate




NAND gate



XNOR gate


AND Gate

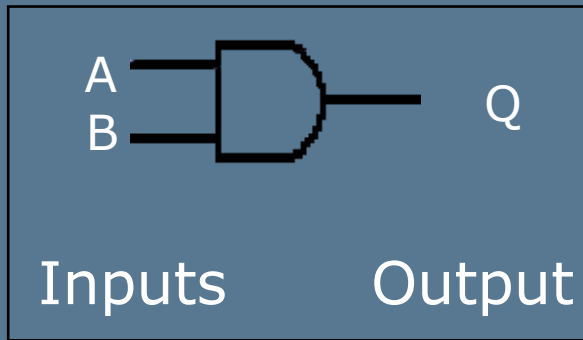

Truth Table

Inputs		Output
A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1


OR Gate

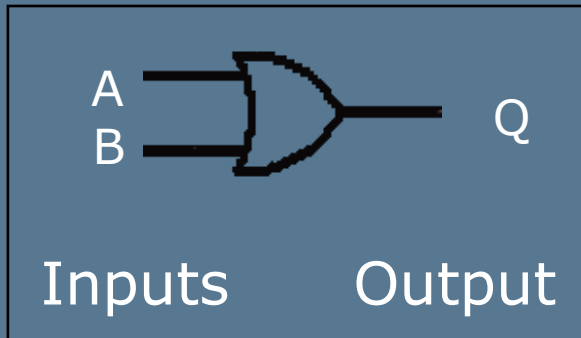

Truth Table

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

NOT Gate

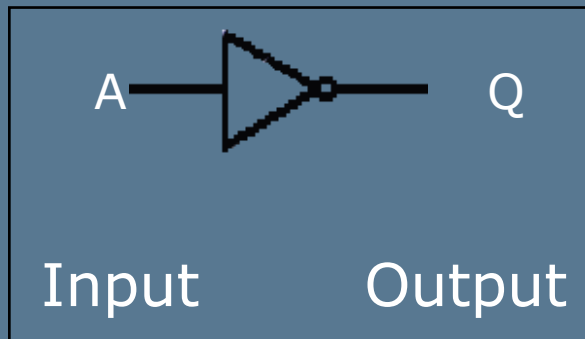

Truth Table

Input	Output
A	Q
0	1
1	0



Other Gates

- Why use?
 - Saves cost
 - Saves space
 - Saves time



Other Gates


- Why use?

- Saves cost
- Saves space
- Saves time

- Types

- NAND gate
- NOR gate
- XOR gate
- XNOR gate


NAND Gate

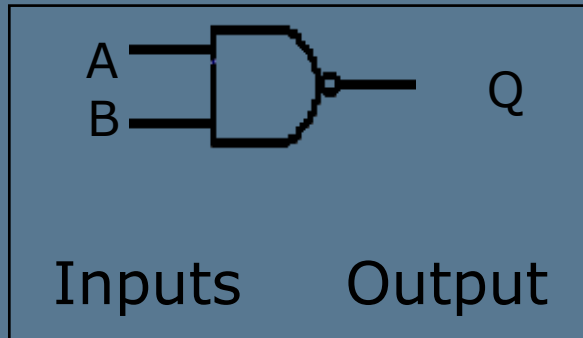

Truth Table

Inputs		Output
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0


NOR Gate

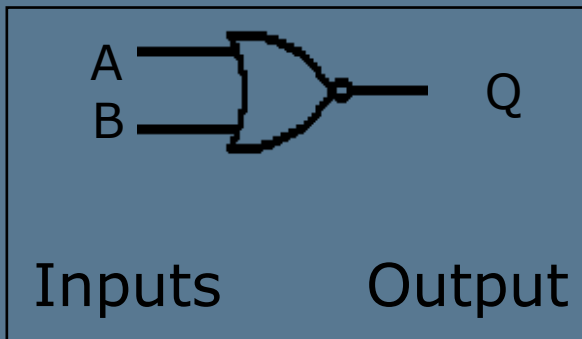

Truth Table

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0


Exclusive-OR Gate

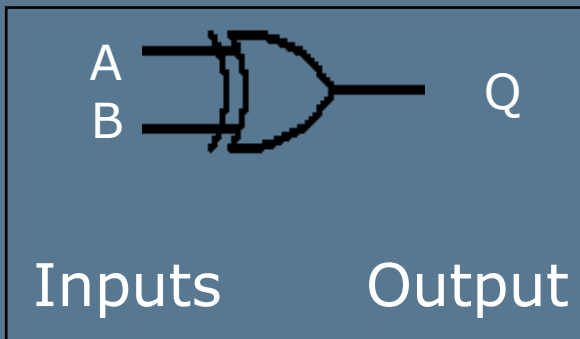

Truth Table

Inputs		Output
A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

XNOR Gate

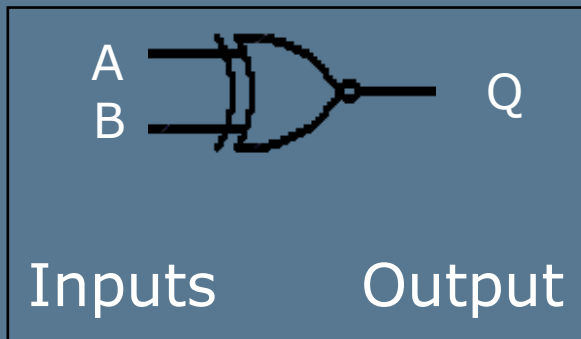

Truth Table

Inputs		Output
A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1



Digital Logic gates

- Draw the logic diagram of the function
 $F = A + B'C$

A

B

C


Digital Logic gates

- Draw the logic diagram of the function $F = A + B'C$




Digital Logic gates

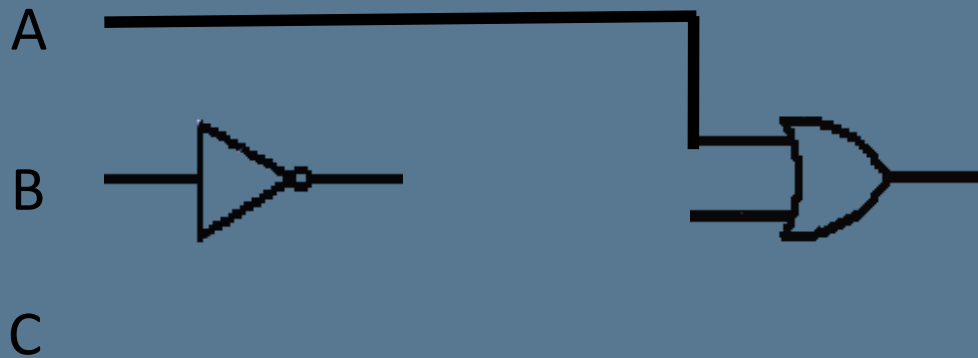- Draw the logic diagram of the function $F = A + B'C$




Digital Logic gates

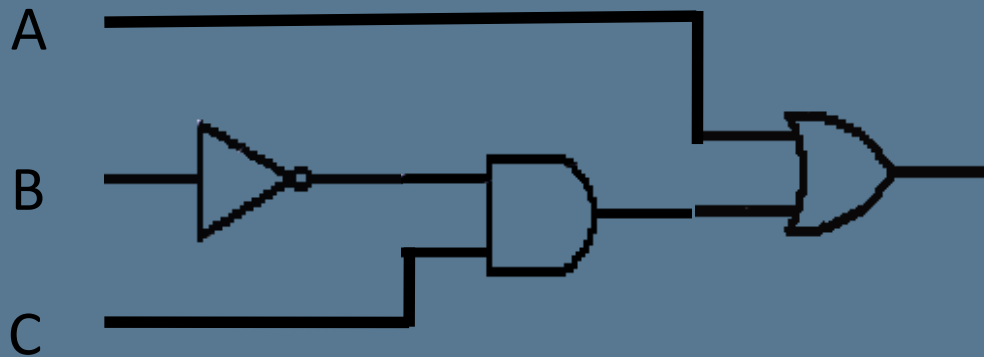- Draw the logic diagram of the function $F = A + B'C$




Digital Logic gates

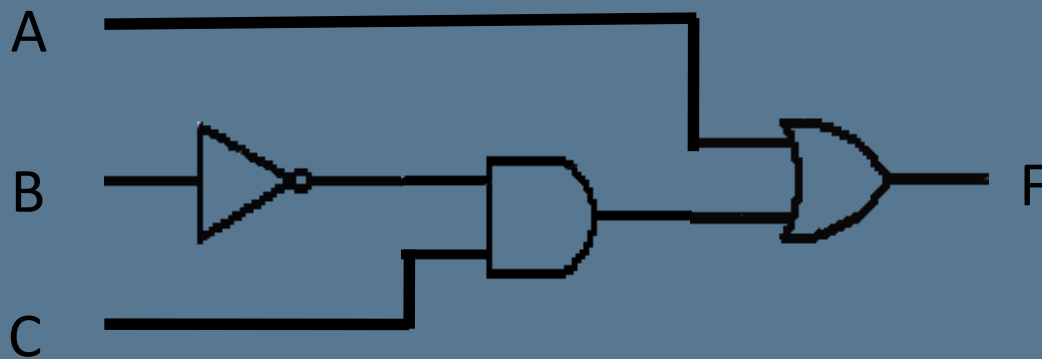- Draw the logic diagram of the function $F = A + B'C$





Universality of NAND gate

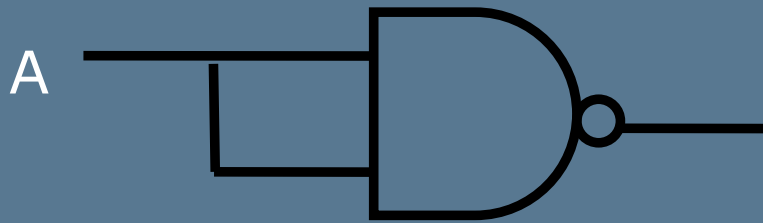


$$Q = (A.A)'$$

Universality of NAND gate

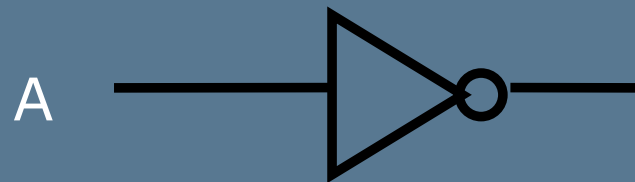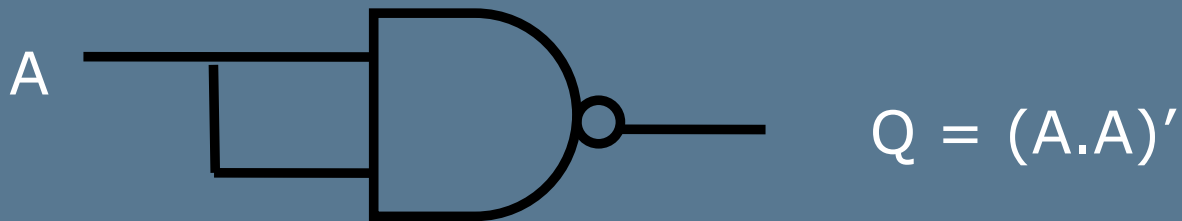


$$Q = A'$$

Universality of NAND Gate

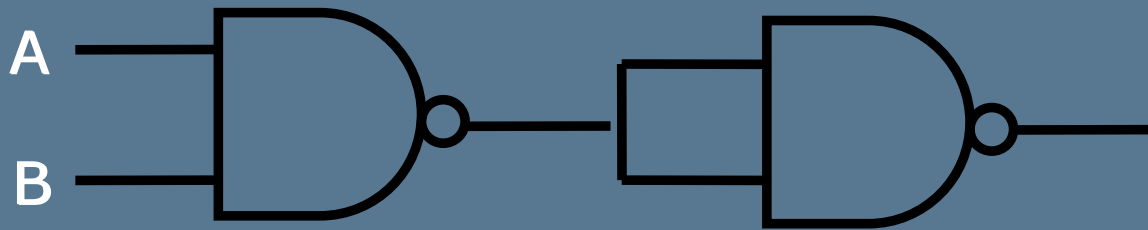


Universality of NAND Gate


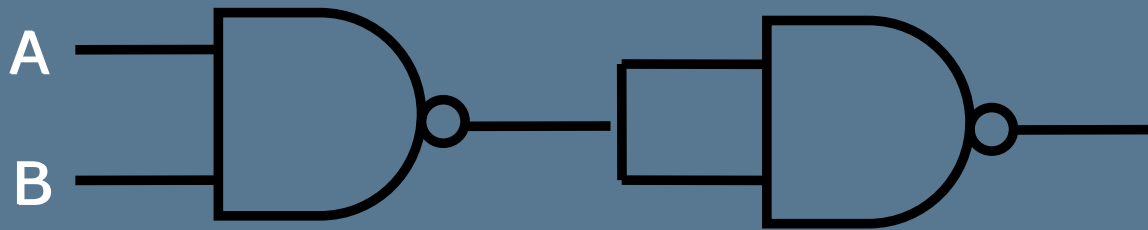


$$Q = ((AB)' (AB)')'$$

Universality of NAND Gate

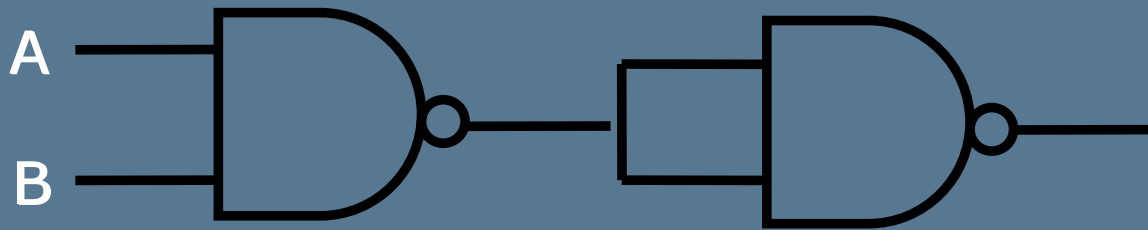


$$Q = ((AB)' (AB)')'$$

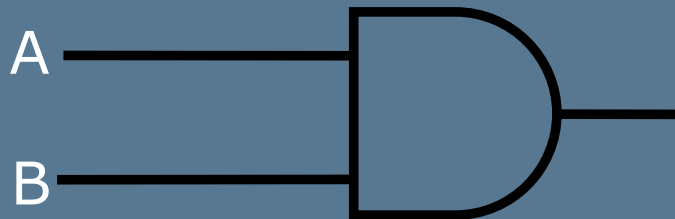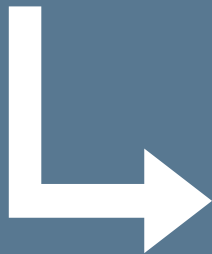


$$Q = AB$$




Universality of NAND Gate

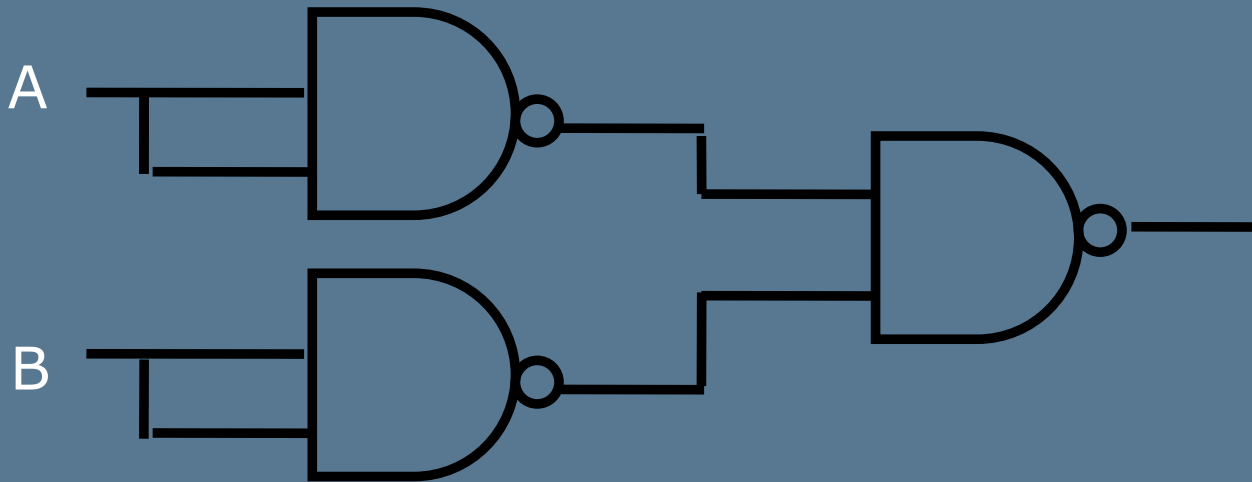


Universality of NAND Gate

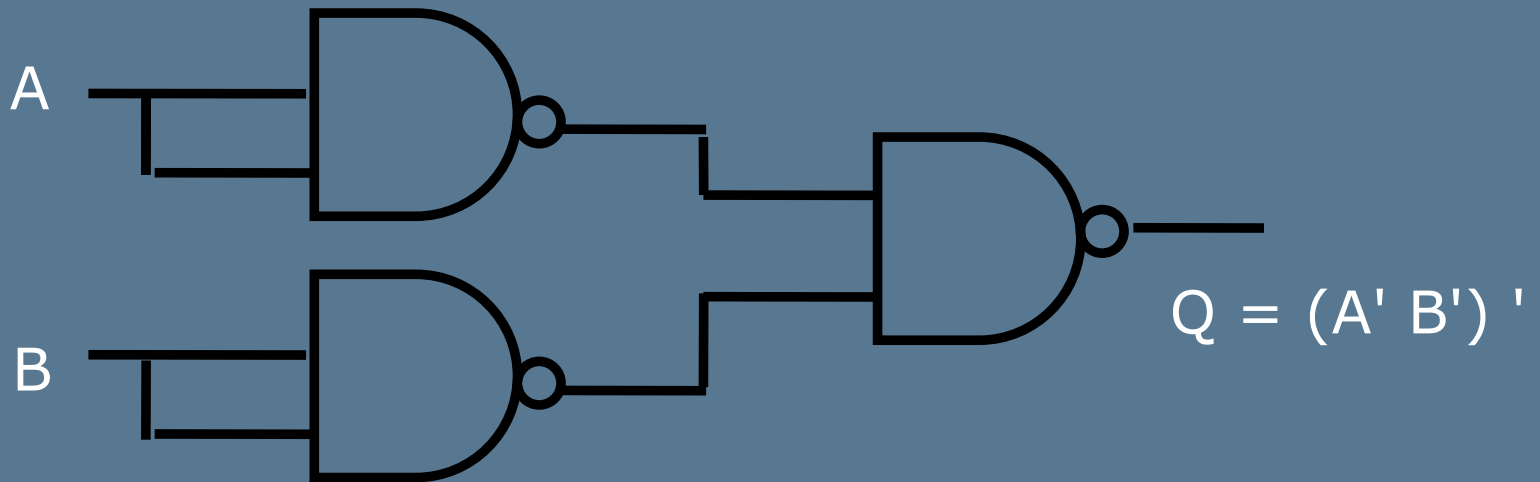

Universality of NAND Gate

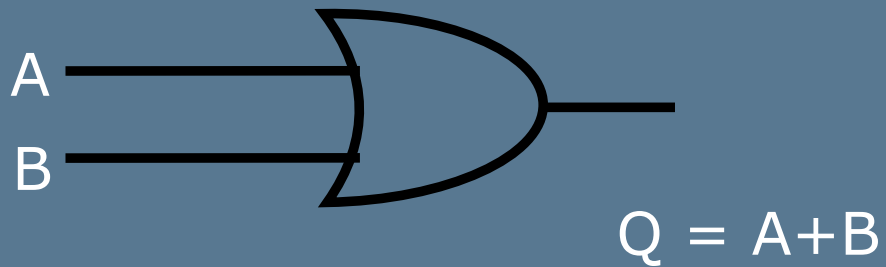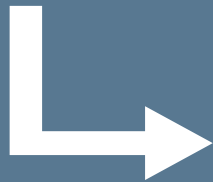
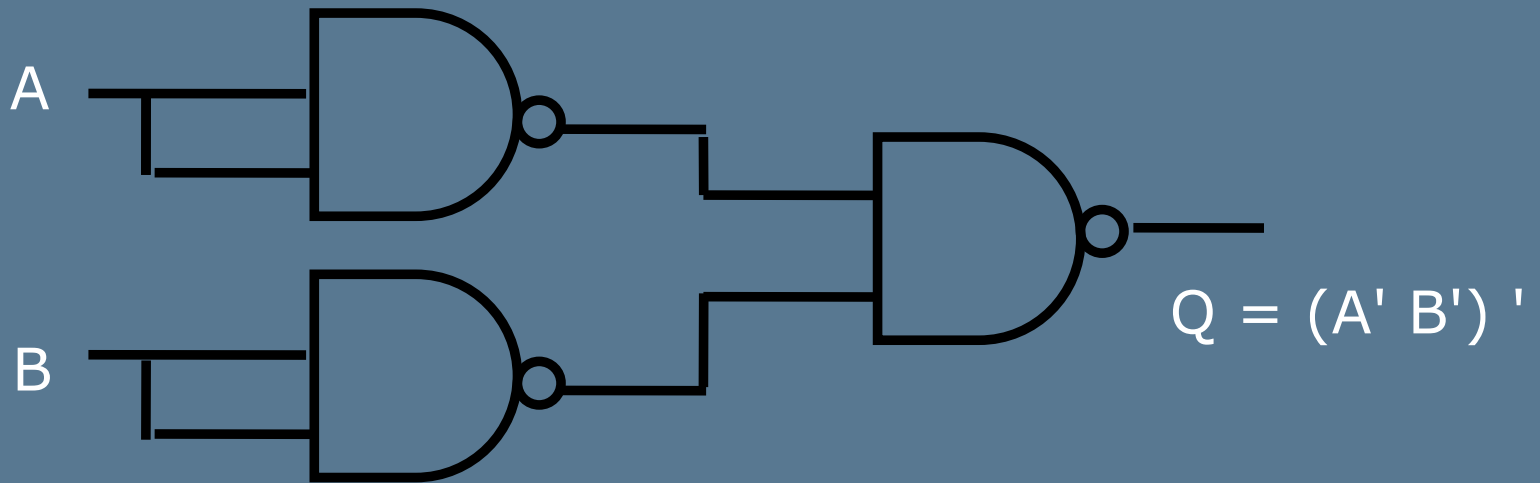


Universality of NOR Gate

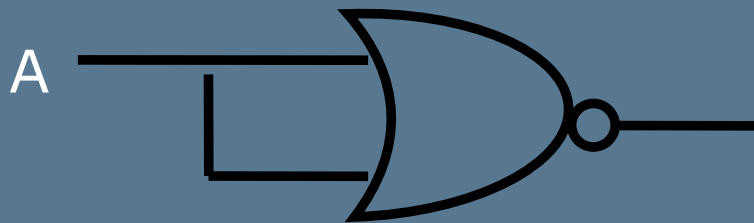


$$Q = (A + A)'$$


Universality of NOR Gate

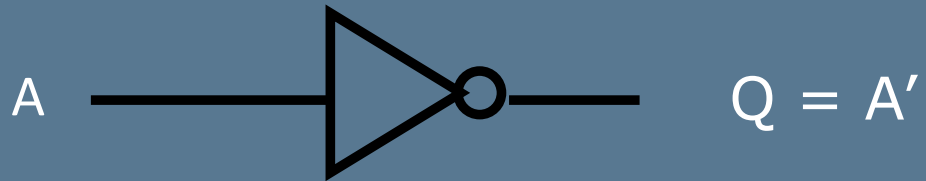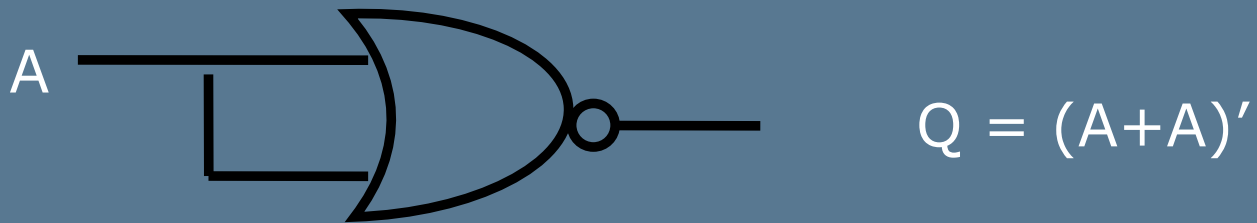

Universality of NOR Gate

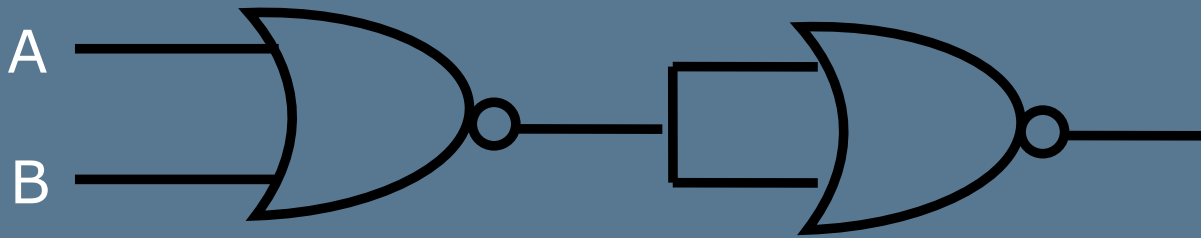


Universality of NOR Gate

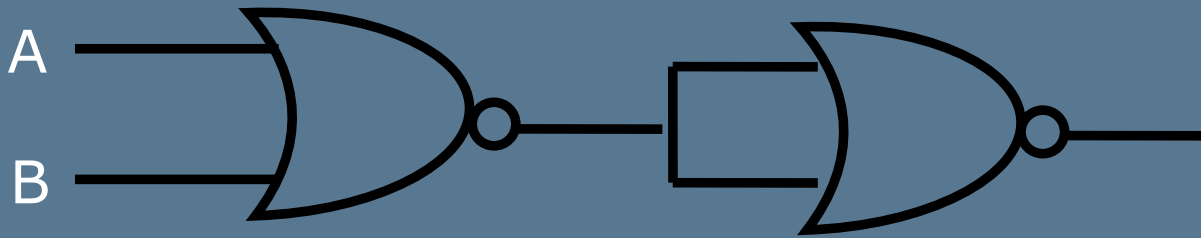


$$Q = ((A+B)' + (A+B)')'$$

Universality of NOR Gate

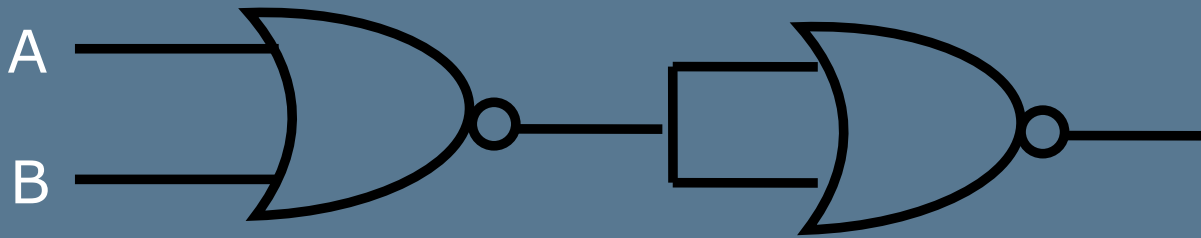


$$Q = ((A+B)' + (A+B)')'$$

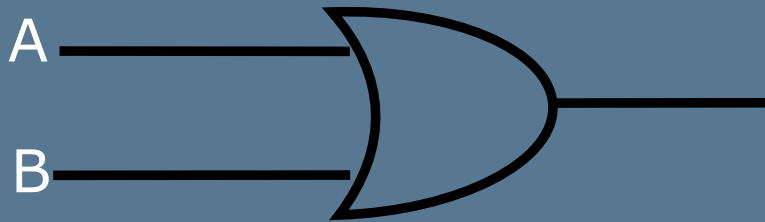


$$Q = A+B$$




Universality of NOR Gate

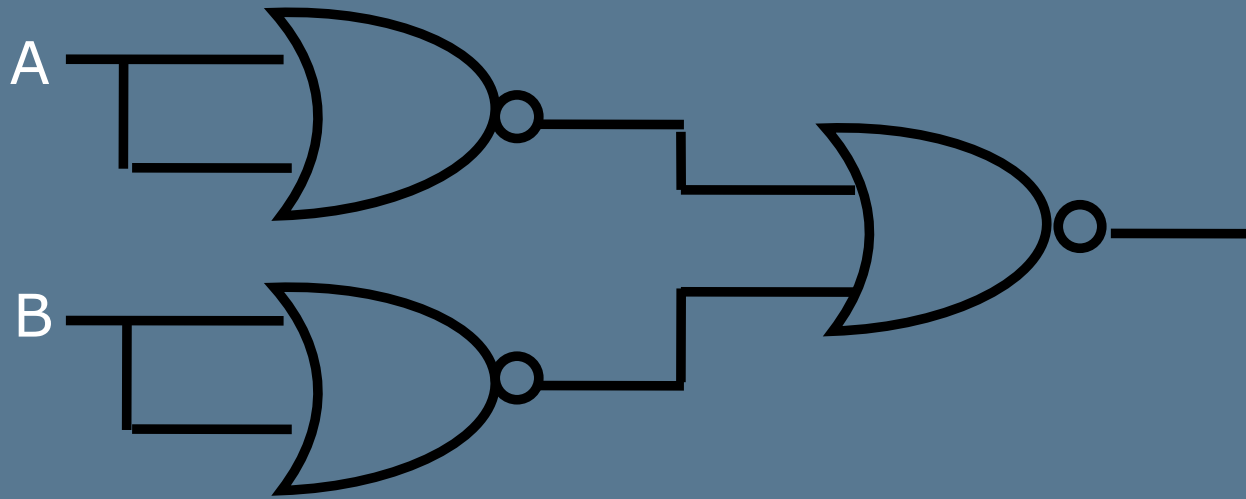

Universality of NOR Gate

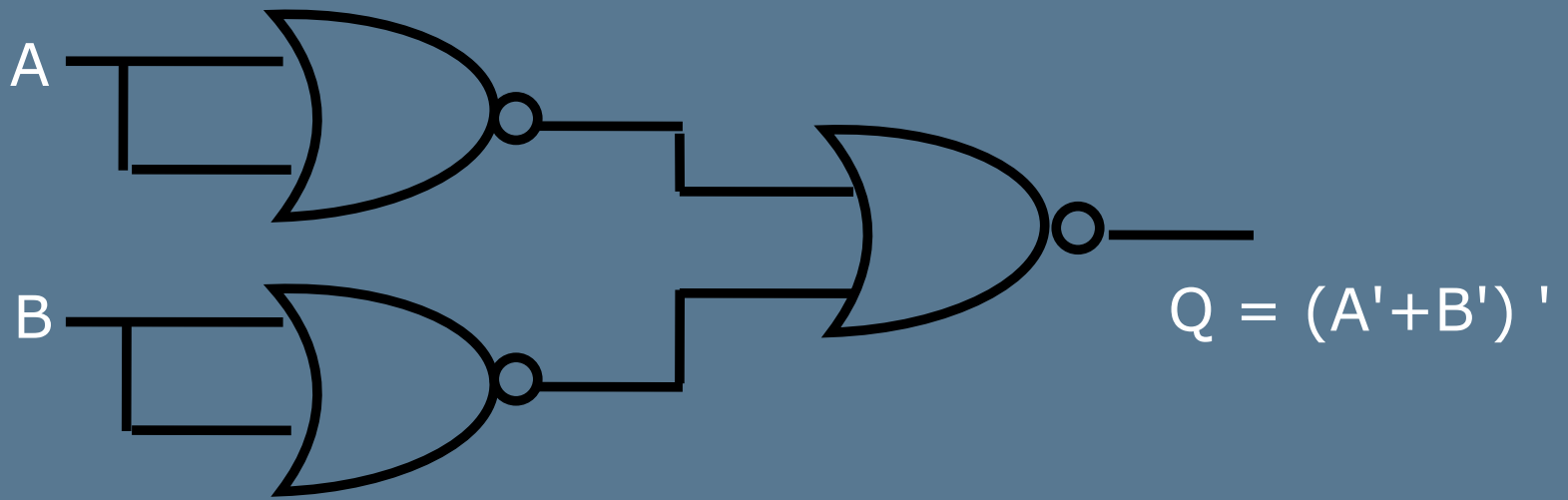

Universality of NOR Gate

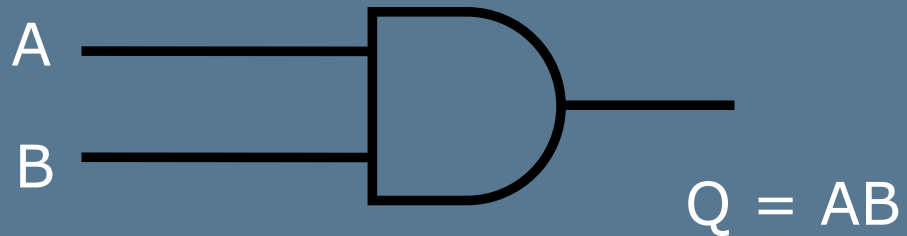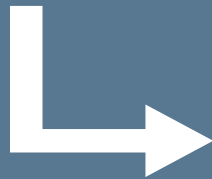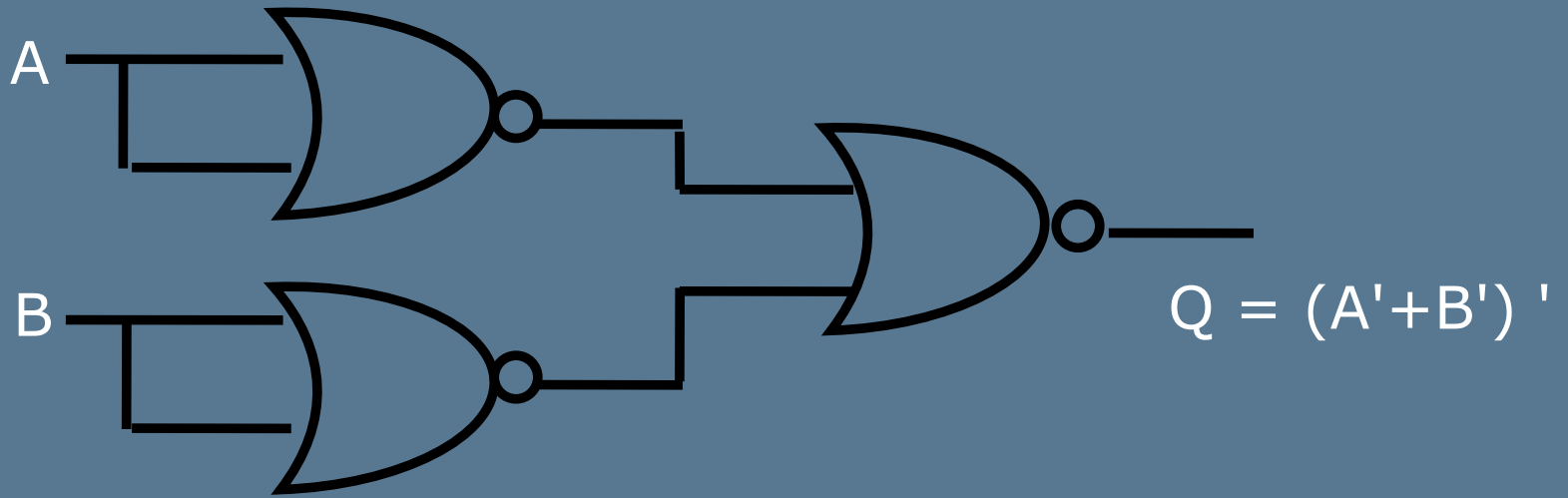

Real Gates

- Logic gates are in integrated form
 - built within a solid piece of silicon called an IC (integrated circuit)



- Several gates are included in a single plastic moulding



IC Families

- Transistor-Transistor Logic (TTL)
- Emitter Coupled Logic (ECL)
- Complementary Metal-Oxide-Semiconductor (CMOS)



Levels of IC

- Small-scale Integration

- ICs with 1 to 10 gates

- Medium-scale Integration

- ICs with 10 to 100 gates

- Large-scale Integration

- ICs with 100 to 1000s of gates

- Very large-scale Integration

- ICs with 1000s to millions of gates