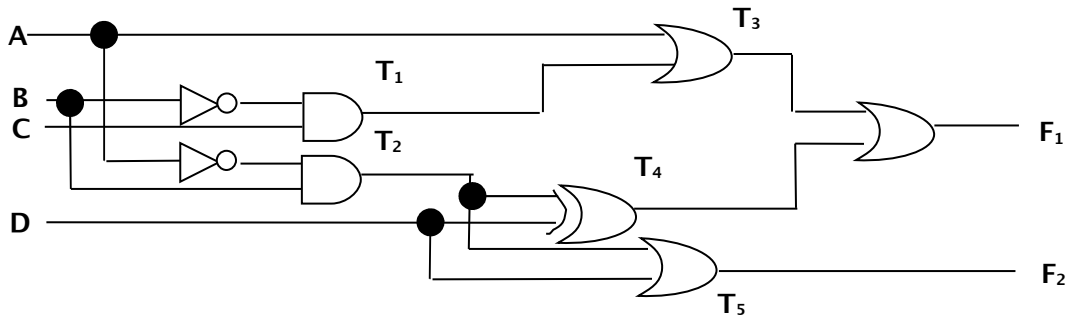


CMSC 130 – Logic Design and Digital Computer Circuits
Handout # 6: ANALYSIS OF COMBINATIONAL CIRCUITS

Derivation of Boolean Functions From a Logic Diagram

1. Label all gate outputs that are a function of input variables with arbitrary symbols.
2. Label the gates that are a function of input variables and previously labeled gates with different arbitrary symbols. Find the boolean functions for these gates.
3. Repeat step 2 until the outputs of the circuits are obtained in terms of the input variables.




Logic Diagram 1

Boolean Functions:

$$\begin{aligned} T_1 &= B'C \\ T_2 &= A'B \\ T_3 &= A + T_1 = A + B'C \\ T_4 &= T_2 \text{ xor } D = (A'B) \text{ xor } D \\ T_5 &= T_2 + D = A'B + D \\ F_1 &= T_3 + T_4 = A + B'C + (A'B) \text{ xor } D \\ F_2 &= T_5 = A'B + D \end{aligned}$$

Derivation of the Truth table

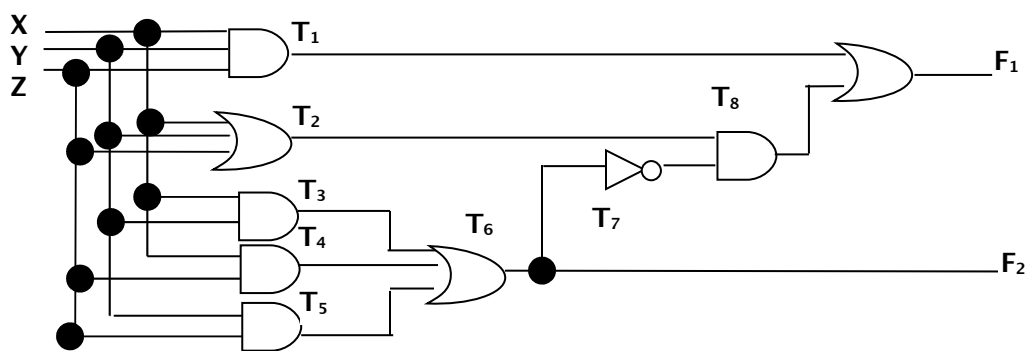1. Determine the number of input variables in the circuit. List binary numbers 0 to $2^n - 1$, where n = number of inputs.
2. Label the outputs of selected gates with arbitrary symbols.
3. Obtain the truth table for the outputs of those gates that are a function of the input variables only.
4. Proceed to obtain the truth table for the outputs of those gates that are a function of previously defined values until the columns for all the outputs are determined.



Logic Diagram 2

Truth Table:

X	Y	Z	T1	T2	T3	T4	T5	T6	T7	T8	F1	F2
0	0	0	0	0	0	0	0	0	1	0	0	0
0	0	1	0	1	0	0	0	0	1	1	1	0
0	1	0	0	1	0	0	0	0	1	1	1	0
0	1	1	0	1	0	0	1	1	0	0	0	1
1	0	0	0	1	0	0	0	0	1	1	1	0
1	0	1	0	1	0	1	0	1	0	0	0	1
1	1	0	0	1	1	0	0	1	0	0	0	1
1	1	1	1	1	1	1	1	1	0	0	1	1